

ELECTRICAL ENGINEERING



Carlin	Page
Date	/ /

Units -

- 1) A.C. Circuits
- 2) D.C. Circuits
- 3) Magnetic Circuits
- 4) Transformers
- 5) Rotating Electrical Machines

Electricity

Generation

(G)

Transmission

(T_x)

Distribution

11 KV, 3-φ

Phase


Max^m

765 KV / 400 KV / 132 KV / 66 KV / 33 KV

← T_x →

33 KV / 11 KV / 440 V

← Distribution →

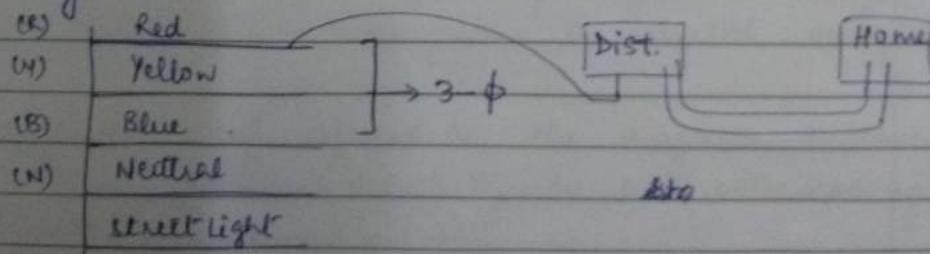5-Wire System:

Neutral → used for return path

Neutral & grounding (or Earthing) are different.

Resistor is a device & resistance is its property to oppose flow of charge.

Camlin Page
Date / /

Standard Rating -

230V, 50Hz, Single-Phase (1- ϕ), A.C Supply

3-Pin

o → Earthing

Line o
 Neutral

Definitions - (Unit - 1)



- | | |
|----------------------------|--|
| 1) Current | 11) Permeability |
| 2) Voltage | 12) Permittivity |
| 3) Electrical Power | 13) Permeance |
| 4) Electrical Energy | 14) Ohm's Law |
| 5) Potential Difference | 15) Series and parallel circuit |
| 6) Potential | 16) Current division and voltage division rule |
| 7) Charge | |
| 8) Resistance, Resistivity | |
| 9) Conductance | |
| 10) Conductivity | |

Unit - I
A.C. Circuits

Generation of EMF -

$$e = -N \frac{d\phi}{dt} \quad (\text{Lenz's Law})$$

$$E = E_m \sin \omega t$$

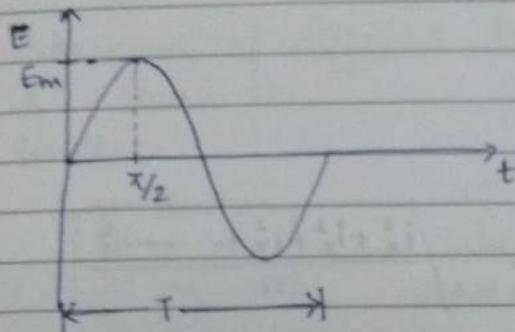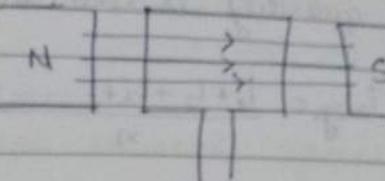

I :- Time taken to complete one cycle

A :- Max^m value attained during cycle is amplitude

f :- No. of cycles produced in one second.

Phase & Phase difference:-

The phase of an alternating quantity at an instant is defined as the fractional part of a cycle through which the quantity has advanced from a selected origin.

Phase difference is defined as the angular displacement b/w maximum values (+/-) of the two alternating quantities having same frequency.


Peak Value:-

Maximum value attained by any alternating quantity during one complete cycle.

(Max^m value, crest value)

Average Value :-

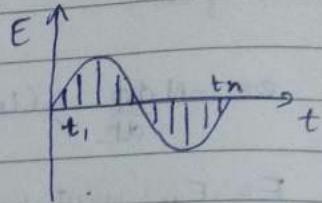Arithmetic average of all the instantaneous values is over one complete cycle.




NOTE :- Avg. value of a sinusoidal quantity is zero (always).

$$i_{avg} = \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$

RMS or Effective value :-

$$\text{Mathematically, } I_{rms} = \sqrt{\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}}$$

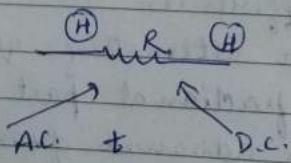The steady current which when flows through a resistor of $\text{10}\Omega$ known resistance for a given time produces the same amount of heat as produced by A.C. quantities which when supply to the same resistor for the same time.



Form Factor-

It is the ratio of RMS value and avg. value.

$$F.F. = \frac{I_{rms}}{I_{avg}} \text{ or } \frac{E_{rms}}{E_{avg}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}, \quad I_{avg} = \frac{2I_m}{\pi}$$

$$F.F. = \frac{I_{rms} \times \pi}{\sqrt{2} \cdot I_{avg}} = \frac{\pi}{2\sqrt{2}} = 1.11$$



- Form factor for a sinusoidal quantity is 1.11.

Peak Factor:-


It is the ratio of maximum value to the RMS value.

$$P.F. = \frac{I_m}{I_{rms}} \text{ or } \frac{E_m}{E_{rms}}$$

$$P.F. = \sqrt{2} = 1.414$$

Behaviour of different Electrical elements against an A.C. Source :-

1) Resistor:-

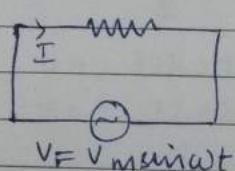

Let a purely resistive network, which is supplied by an alternating voltage $V = V_m \sin \omega t$.

The instantaneous value of current flowing in the resistor, $I = \frac{V}{R}$ (By Ohm's Law)

$$I = \frac{V_m \sin \omega t}{R} \quad \text{--- (1)}$$

For maximum value of current, $\omega t = 90^\circ$ or $\sin \omega t = 1$

$$I_m = \frac{V_m}{R}$$

Put this value of I_m in eqⁿ(1)

$$I = I_m \sin \omega t$$


From the eqⁿ's of V & I it is analysed that both are in same phase, hence for a purely resistive network current is always in phase with voltage.

Instantaneous Power, $P = V, I$

$$P = (V_m \sin \omega t) (I_m \sin \omega t)$$
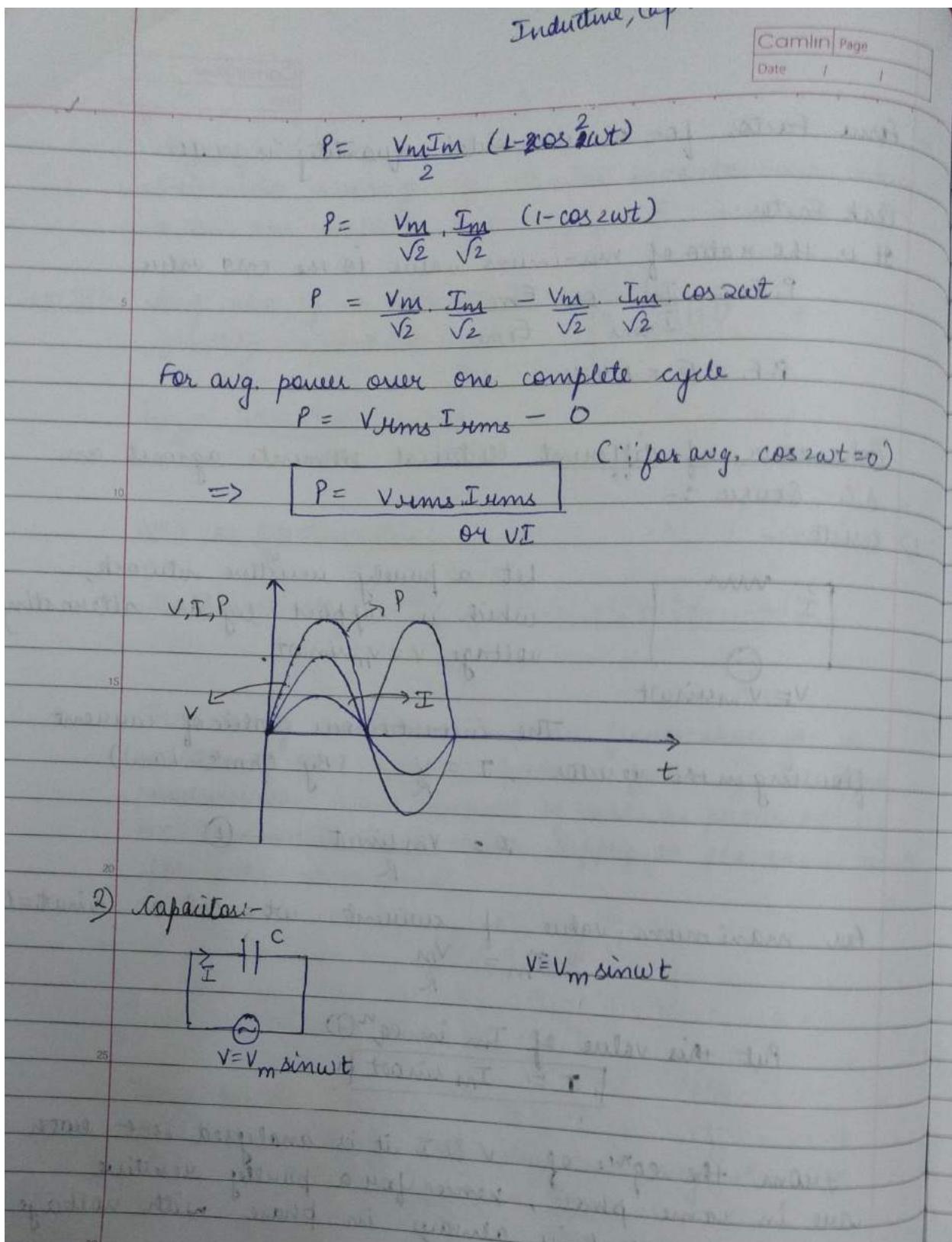
$$P = \frac{V_m I_m}{2} (\sin^2 \omega t)$$





Camlin	Page
Date	/ /

- Q-1) An A.C. circuit consist of pure resistance of 10 ohms and is connected across a supply of $\frac{230}{\sqrt{2}}$ volts, 50Hz. Calculate -
 i) Current
 ii) RMS value (by default)
 iii) Power consumed
 iv) Eqn for voltage and current.

Sol:- i) $I = \frac{V}{R} = \frac{230 \sin(2\pi \times 50 \times t)}{10} = 23 \sin(100\pi t)$

$V = \frac{230\sqrt{2}}{\sqrt{2}} \sin 100\pi t$ ii) $I = \frac{V}{R} = \frac{230}{10} = 23A$

iii) $P = V_{rms} \cdot I_{rms}$
 $= 230 \times 23 = 5290W$

$V = 325.27 \sin 100\pi t$

$I = 32.527 \sin 100\pi t$

- Q-2) An inductive coil having negligible resistance & 0.1 Henry inductance is connected across 200V, 50Hz supply. Find
 i) Inductive reactance ii) RMS value of current iii) Power
 iv) Eqn for voltage & current

Sol:-

i) $X_L = \omega L = 2\pi f L = 2\pi \times 50 \times 0.1 = 10\Omega$

ii) $I_{max} =$

iii) Power = 0 (Avg. Power)

iv) $V = 200\sqrt{2} \sin 100\pi t = 282.84 \sin 100\pi t$

$I = \frac{282.84}{10\Omega} \sin(100\pi t - \frac{\pi}{2})$

$= 9 \sin(100\pi t - \frac{\pi}{2})$

v) $I = \frac{V}{X_L} = \frac{200}{31.4} = 6.37 A$



- Q-3) A capacitor has a capacitance of $30\mu F$. Find its
 i) Capacitive reactance for frequencies of 25 & 50 Hz.
 ii) In each case, find the current if the supply voltage
 is 440V.


Sol:-

$$\text{i)} X_C = \frac{1}{\omega C} = \frac{10^6}{2\pi \times 25 \times 30} = \frac{1000}{50 \times 3 \times \pi} = \frac{2000}{3\pi} = 212.21 \Omega$$

$$\text{ii)} X_C = \frac{1}{\omega C} = \frac{10^6}{2\pi \times 50 \times 30} = \frac{1000}{3\pi} = 106.1 \Omega$$

$$\text{i)} I = \frac{440}{212.21} = 2.07 \text{ A}$$

$$\text{ii)} I = \frac{440}{106.1} = 4.14 \text{ A}$$

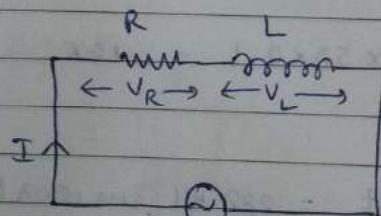A.C. Series circuits:-(I) R-L Combination (Circuit) :-

$$V_R = IXR$$


$$V_L = IXX_L$$

(where $X_L = 2\pi fL$)

$$V = V_m \sin \omega t$$

In right angled $\triangle OAB$

$$V = \sqrt{V_R^2 + V_L^2}$$

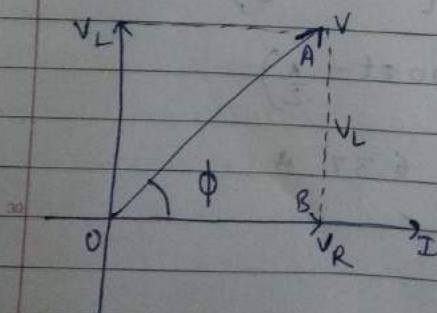


$$V = \sqrt{I^2 R^2 + I^2 X_L^2}$$

$$V = I \sqrt{R^2 + X_L^2}$$

$$I = \frac{V}{\sqrt{R^2 + X_L^2}}$$



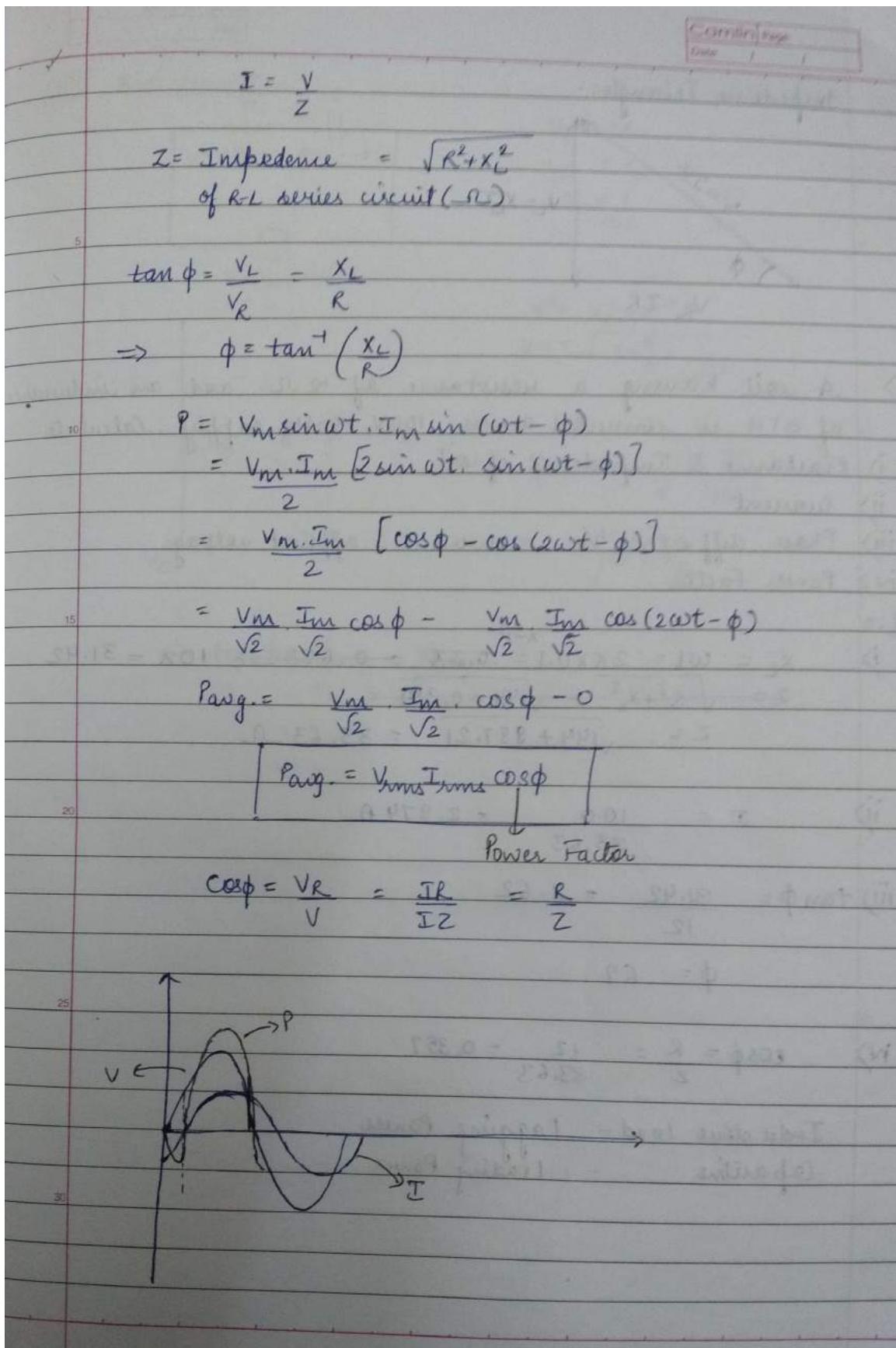

R008, REC 001,
Date / / Page / /

Impedance Triangle:-

Q-1) A coil having a resistance of $12\ \Omega$ and an inductance of $0.1\ H$ is connected across $100V, 50\ Hz$ supply. Calculate

- Reactance & Impedance of coil
- Current
- Phase difference b/w current & applied voltage
- Power Factor

Sol:-

- $$X_L = \omega L = 2\pi \times 0.1 = \cancel{0.2\pi} \times 50 = 0.628 \approx 10\pi = 31.42$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{144 + 987.21} = 33.63\ \Omega$$
- $$I = \frac{100}{33.63} = 2.974\ A$$
- $$\tan \phi = \frac{31.42}{12} = 2.62$$

$$\phi = 69$$
- $$\cos \phi = \frac{R}{Z} = \frac{12}{33.63} = 0.357$$

Inductive load - Lagging Power
Capacitive - Leading Power



Camlin Page
Date / /

(II) R-C circuit :-

$V = V_m \sin(\omega t)$

$V_R = IR$

$V_L = IX_C$

$X_C = \frac{1}{\omega C}$

$V^2 = V_R^2 + V_C^2$

$V = I \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$

$I = \frac{V}{\sqrt{R^2 + \frac{1}{(\omega C)^2}}}$

$Z = \sqrt{R^2 + X_C^2}$

$\tan \phi = \frac{V_C}{V_R} = \frac{X_C}{R}$



Camilin Page
Date / /

(III) R-L-C circuit :-

$$V = V_m \sin \omega t$$

$$V_R = IR$$

$$V_C = IX_C \quad (X_C = 1/\omega C)$$

$$V_L = IX_L \quad (X_L = \omega L)$$

In $\triangle OAB$,

$$V^2 = V_R^2 + (V_L - V_C)^2$$

$$V = \sqrt{I^2 R^2 + (IX_L - IX_C)^2}$$

$$V = I \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$I = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R} = \frac{1}{R} \left(\omega L - \frac{1}{\omega C} \right)$$

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t - \phi)$$

$$P = V_{rms} I_{rms} \cos \phi$$

$$P.F. = \cos \phi = \frac{R}{Z}$$

i) $X_L > X_C \rightarrow$ Inductive ckt (lagging)

ii) $X_C > X_L \rightarrow$ Capacitive ckt (leading)

iii) $X_C = X_L \rightarrow$ Resistive ckt



Comlin	Page
Date	/ /

Q- A resistance of $15\ \Omega$ & $C = 150\ \mu F$ are connected in series across $230V, 50\text{Hz}$ supply. Calculate:-

- Z
- I
- $\cos\phi$
- $\tan\phi$
- Power consumed.

Sol:-

$$i) Z = \sqrt{R^2 + X_C^2} = 25.99\ \Omega$$

$$X_C = \frac{1}{2\pi f C} = 21.23\ \Omega$$

$$ii) I = \frac{V}{Z} = \frac{230}{25.99} = 8.84\ A$$

$$iii) \cos\phi = \frac{R}{Z} = \frac{15}{25.99} = 0.577 \text{ leading}$$


$$iv) \phi = \cos^{-1}(0.577) = 54.75^\circ$$

$$v) P = VI \cos\phi \\ = 1174.9\ W$$

Q- A coil of resistance $10\ \Omega$ & inductance $0.1\ H$ is connected in series with a condenser of capacitance $150\ \mu F$ across $200V, 50\text{Hz}$ supply. Determine

- Z
- I
- $\cos\phi$
- Voltage across coil
- Voltage across condenser.

Sol:-

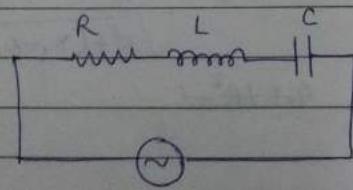

$$i) Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{100 + \left(2\pi \times 50 \times 0.1 - \frac{10^6}{2\pi \times 50 \times 150}\right)^2}$$

$$= \sqrt{100 + \left(10\pi - \frac{10^6}{1000 \times \pi \times 15}\right)^2}$$

$$= \sqrt{100 + (31.42 - 21.22)^2} = \sqrt{204.04} = 14.28\ \Omega$$



$$\text{ii) } I = \frac{V}{Z} = \frac{200}{14.28} = 14 \text{ A}$$

$$\text{iii) } \cos \phi = \frac{R}{Z} = \frac{10}{14.28} = 0.7 \text{ lagging } (X_L > X_C)$$

$$\text{iv) } V_C = X_C \times I = \frac{1}{\omega C} \times I = \frac{14 \times 10^6}{2 \pi \times 50 \times 150} = \frac{14 \times 10^6}{1080 \times 150} \\ = 297.08 \text{ V}$$

$$\text{v) } V_{coil} = \sqrt{R^2 + X_L^2} \times I = \sqrt{100 + 987.21} \times 14 \\ = \sqrt{1087.21} \times 14 \\ = 461.62 \text{ V}$$

Q.- A coil of power factor 0.8 is in series with a $100\mu F$ capacitor when connected to 50Hz supply, the voltage across capacitor is equal to voltage across coil. Find the values of resistance and inductance.

Sol:-

$$\cos \phi = 0.8, f = 50 \text{ Hz}$$

$$V_C = V_{coil}$$

$$IX X_C = IX \sqrt{R^2 + X_L^2}$$

$$X_C^2 = R^2 + X_L^2$$

$$\frac{1}{\omega^2 C^2} = R^2 + \omega^2 L^2$$

$$100 \times 10^{-6}$$

$$10^{-4}$$

$$A, \frac{10^8}{39.48} = R^2 + 39.48 L^2$$

$$\cos \phi = \frac{R}{Z}$$

$$0.8 = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$0.8(R^2 + (X_L - X_C)^2)$$



Comlin	Page
Date	/ /

Types of Power:-

1) Apparent Power-

Product of RMS value of applied voltage and circuit current.
It is also called wattless or ideal Power. It is represented by

$$S = \text{Voltage} \cdot \text{Current}$$

$$= (I Z) \cdot I$$

Unit:- VA (volt Ampere)

→ It is calculated when power factor of the ckt. is unknown.

2) Active Power:-

It is the power which is actually dissipated in the ckt-
(especially resistance).

$$P = VI \cos \phi$$

$$= I^2 R \text{ Watts}$$

3) Reactive Power:-

It is the power developed in the reactance of the circuit.


It is represented by

$$Q = VI \sin \phi$$

$$= I^2 X_L$$

Unit:- VAR (volt Ampere reactive)
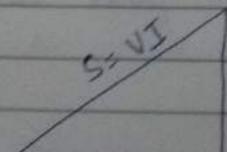
$$\boxed{S = P + jQ} \rightarrow \text{Complex Form Notation}$$



$$P = VI \cos \phi$$



C → R. Power generator / supplier
 L → R. Power Absorber

Camlin	Page
Date	/ /

Power Factor:-

It is the cosine of angle b/w voltage and current or
 It is the ratio of resistance and impedance of the circuit &
 It is the ratio of Active power to the Apparent Power.

I) When $\phi = 0^\circ$:- $\cos\phi = 1$
 Purely Resistive Network

II) When $\phi = 90^\circ$:- $\cos\phi = 0$
 The circuit may be inductive or capacitive.

III) When there is a combination of RC, RLC or RL, the power factor lies b/w 0 and 1.

Factors:-

By the relation $\frac{P}{VI} = \cos\phi$, for a fixed power at constant voltage I is inversely proportional to $\cos\phi$.
 So, if the circuit power factor is low, circuit will draw heavy current from the mains which results in following disadvantages-

- 1) Greater conductor size
- 2) Poor Efficiency
- 3) Larger voltage drop and results in poor regulation
- 4) Larger \downarrow KVA rating of equipments.

(Kilo Volt Amp.)




Resonance:-

Resonance in an AC circuit is a phenomena in which, may be resistances or currents of inductive and capacitive loads would be equal.

Resonance is of 2 types-

- 1) Series
- 2) Parallel

Series Resonance:-

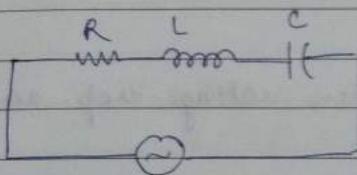

In series RLC circuit, when circuit current is in phase with applied voltage, then it is said to be in series resonance. Under this condition

$$X_L = X_C$$

$$\text{or } X_L - X_C = 0$$

then $Z = R$ (under this condition)

Under series resonance condition, as $Z=R$ the circuit will draw maximum current.

Resonant Frequency:-

$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$

Under series resonance, $X_L = X_C$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$



Effect of Series Resonance -

- 1) At $X_L = X_C$, $Z = R$.
Network / circuit behaves as resistive network and Z of network will be minimum. As current drawn by the network will be max^m, it is sometimes called as Acceptor Circuit.
- 2) As Z will be minimum, then ckt current will be maximum.

$$I_R = \frac{V}{Z} = \frac{V}{R}$$


- 3) Power taken by the network will also be max^m as current will be max^m.

$$P_R = I_R^2 R$$

- 4) As current will be max^m, then voltage drop across L & C will also be maximum.

Applications -

- 1) Radio & TV receivers.
- 2) Tuning circuits.

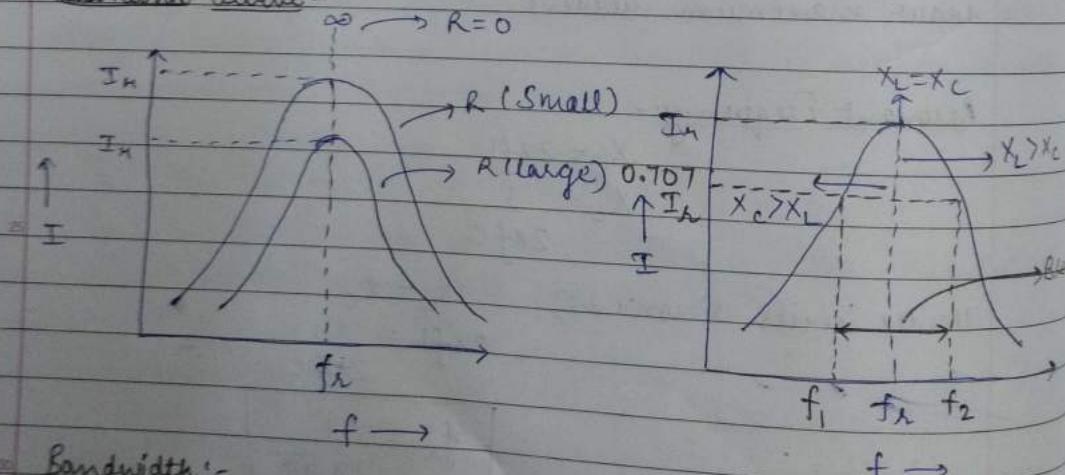Resonance Curve -Bandwidth:-

The range of frequencies over which circuit current is equal to or more than 70.7% of maximum current is known as bandwidth.

B.W. \rightarrow Bandwidth



$$\text{B.W.} = f_2 - f_1$$

f_1 : Lower cut-off frequency
 f_2 : Upper cut-off frequency

Q-factor:-

The factor by which the potential difference across L or C rises to that of applied voltage is called Q-factor.

$$\text{Q-factor} = \frac{V_L \text{ or } V_C}{\text{Applied voltage}}$$

$$V_L = IX_L \quad , \quad V_C = IX_C$$

$$V = IZ = IR$$

$$\text{Q-factor} = \frac{IX_L}{IR} = \frac{X_L}{R}$$

(Quality factor)

$$X_L = \omega_n L$$

$$= 2\pi f_n L$$

$$= 2\pi \times \frac{1}{2\pi\sqrt{LC}} XL = \frac{L}{\sqrt{LC}}$$

$$\text{Q-factor} = \frac{L}{\sqrt{LC}} \times \frac{1}{R} = \frac{1}{R}\sqrt{\frac{L}{C}}$$

Q.1) A choke coil is connected in series with a $200\mu\text{F}$ capacitor with a constant supply voltage of 250V . The current drawn by the network is 50A . When the supply frequency is 100Hz , determine:

i) R & L of choke coil
 sol:-



Camlin Page
Date / /

$C = 100\mu F, I = 50 A, V = 250 V, f = 100 \text{ Hz}$

$\omega = \frac{2\pi f}{\sqrt{L/C}}$

$I_m = \frac{V}{R}$

$R = \frac{V}{I_m} = \frac{250}{50} = 5 \Omega$

$X_L = X_C$

$2\pi f L = \frac{1}{2\pi f C}$

$L = \frac{1}{4\pi^2 f^2 C} = \frac{10^4}{4\pi^2 \times 10^4 \times 10^{-8}} = 112.66$

$V_C = I_m X_C = 50 \times 10^4 \times 10^{-4} = 1397.88$

ii) Voltage across capacitor

iii) Q-factor

$\frac{V_C}{V} = \frac{1}{R \sqrt{\frac{L}{C}}} = \frac{1}{10^4 \sqrt{5 \times 25 \times 10^{-8}}} = 10^4 \sqrt{5} = 142.85 \text{ Hz}$

Q-2) A choke coil having an inductance of 50 mH and resistance of 10Ω is connected in series with a $25 \mu F$ capacitor across 200 V ac supply. Calculate i) resonant freq. ii) current at resonance iii) Q-factor.

i) $f_R = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{50 \times 10^{-3} \times 25 \times 10^{-6}}} = \frac{1}{2\pi \sqrt{5 \times 25 \times 10^{-8}}} = 10^4 \sqrt{5} = 142.85 \text{ Hz}$

Camlin Page
Date / /

ii) $I_L = \frac{200}{10} = 20A$

iii) Q-factor = $\frac{1/\sqrt{L}}{R\sqrt{C}} = \frac{1}{10} \sqrt{\frac{5 \times 10^3}{25 \times 10^6 \times 10^{-3}}} = \frac{1}{10} \sqrt{\frac{5 \times 10^2}{285}} = \frac{1}{10} \sqrt{20} = 0.4472$

Q-3) An AC varies sinusoidal with a frequency of 50Hz has an rms value of 20A. Write down the eqn for instantaneous value and find the value of current at

- 0.025 seconds
- 0.0125 seconds after passing through max^m +ve value.

Sol:

$f = 50\text{Hz}, I = 20A$

$I = 20\sqrt{2} \sin[\omega t] = 28.28 \sin \omega t = \frac{1}{50}$

$\omega = 2\pi f = 100\pi$

$I = 20\sqrt{2} \sin[100\pi t]$

$20\sqrt{2} \sin(100\pi \times 0.0025)$

$20\sqrt{2} \sin\left[\frac{\pi}{2} + \omega t\right]$

$I = 28.28 \sin(100\pi t)$

$I = 28.28 \cos(100\pi t)$

$I = 28.28 \cos(100\pi \times 0.0025)$

Camlin Page
Date / /

Parallel Resonance

An AC circuit containing an inductor and capacitor in parallel then circuit is said to be in parallel resonance when total current is in phase with applied voltage.

The ckt current I_R will only be in phase with supply voltage when $I_C = I_L \sin \phi_L$.

Since, at resonance, the reactive component of current is suppressed, hence current drawn by the network will be minimum. Due to this, value of impedance will be very high.

$$I_C = I_L \sin \phi_L$$

$$X_C \times I = X_L \times I \sin \phi_L$$

$$I_L = \frac{V}{Z_L} = \frac{V}{\sqrt{X_L^2 + R^2}}$$

$$I_C = \frac{V}{Z_C} = \frac{V}{1/\omega C} = V \omega C$$


$$\sin \phi_L = \frac{X_L}{Z_L}$$
~~$$N.W.C = \frac{V}{\sqrt{X_L^2 + R^2}} \times \frac{X_L}{\sqrt{X_L^2 + R^2}}$$~~

$$C (X_L^2 + R^2) = L$$

$$\frac{V}{R} \neq \frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

$$X_C \cdot X_L = Z_L^2$$

$$\frac{V_L}{V_C} = Z_L^2$$

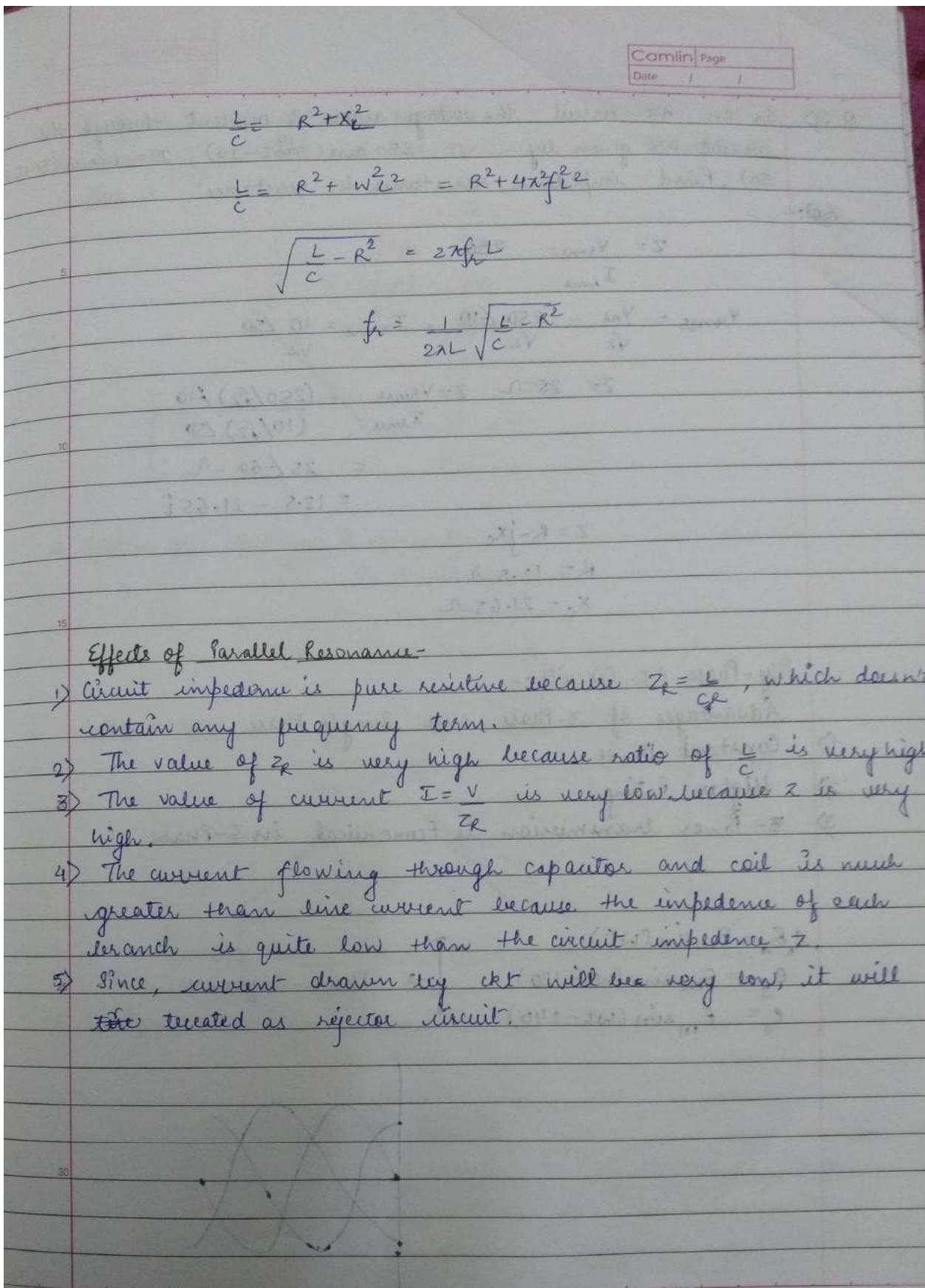

Q-1) In an A.C. circuit the voltage across & current through the circuit are given by $V = 250 \sin(314t - 10)$, $I = 10 \sin(314t + 50)$. Find impedance, resistance & reactance.

Sol:-

$$Z = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{250}{10} \angle 0^\circ$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{250}{\sqrt{2}} \angle 0^\circ, I_{\text{rms}} = \frac{10}{\sqrt{2}} \angle 0^\circ$$

$$\begin{aligned} Z &= 25 \angle 0^\circ \\ Z &= V_{\text{rms}} \angle 0^\circ = \frac{(250/\sqrt{2}) \angle 0^\circ}{(10/\sqrt{2}) \angle 0^\circ} \\ &= 25 \angle 0^\circ \Omega \\ &= 12.5 - 21.65i \end{aligned}$$

$$Z = R - jX_C$$

$$R = 12.5 \Omega$$

$$X_C = 21.65 \Omega$$

Poly-Phase A.C. Circuits :-

Advantages of 3-Phase over Single Phase :-


- 1) Constant Power.
- 2) Higher Rating.
- 3) Power transmission is Economical in 3-Phase.

$$e_R E_R = E_m \sin(\omega t)$$

$$e_Y = E_m \sin(\omega t - 120^\circ)$$

$$e_B = E_m \sin(\omega t - 240^\circ)$$

→ Phase Sequence

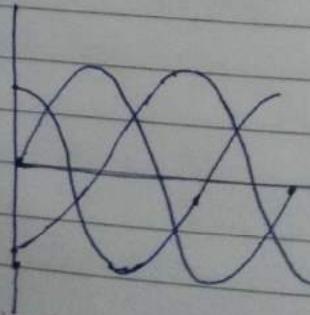


Comlin	Page
Date	/ /

Inter-connection of three phases:-

(i) Star or Y-connection and (ii) Delta or Mesh Connection

Star :-

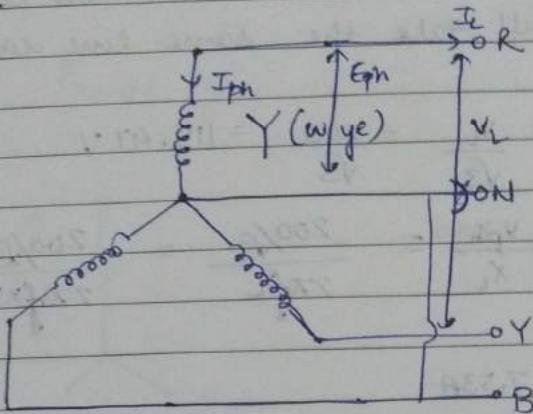


* Relation b/w Voltages & Current :-

$$V_L = \sqrt{3} V_{ph}$$

and $I_L = I_{ph}$

Delta or Mesh :-

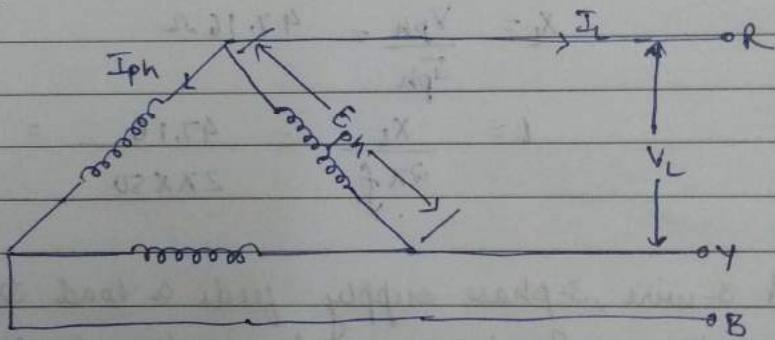

* Relation b/w Voltages & Current :-

$$V_L = V_{ph}$$

and $I_L = I_{ph} \cdot \sqrt{3}$

Q-1) Three inductive coils each of inductance 50 mH are connected in star to a 3-phase 200V, 50Hz supply. Calculate the inductance of each coil when connected in Δ to the same supply & will take the same line current.

Sol:-

$$\text{Star: } V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{200}{\sqrt{3}} = 115.47 \text{ V}$$

$$I_{ph} = \frac{V_{ph}}{X_L} = \frac{200/\sqrt{3}}{2\pi f L} = \frac{200/\sqrt{3} \times 10^3}{2\pi \times 50 \times 50}$$

$$I_L = I_{ph} = 7.53 \text{ A}$$

Delta:-

$$I_{ph} = \frac{I_L}{\sqrt{3}} = 4.24 \text{ A}$$

$$V_{ph} = V_L = 200 \text{ V} \\ (\text{given})$$

$$X_L = \frac{V_{ph}}{I_{ph}} = 47.16 \Omega$$


$$L = \frac{X_L}{2\pi f} = \frac{47.16}{2\pi \times 50} = 0.15 \text{ H}$$

Q-2) A 3-wire, 3-phase supply feeds a load consisting of 3 resistors. By how much is the load reduced if one of the resistors are removed, when the load is in
 i) star
 ii) Delta

Sol:-

i) $P = \frac{(V_{ph})^2}{R}$ in one phase


$$P_{3-\phi} = \frac{3(V_{ph})^2}{R}$$

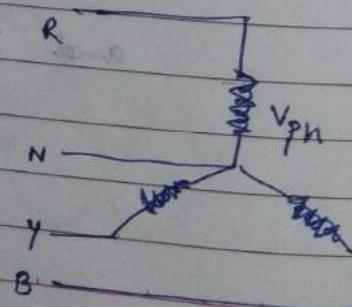

Camlin	Page
Date	/ /

$$P_{3-\phi} = \frac{3 \left(\frac{V_L}{\sqrt{3}} \right)^2}{R}$$

$$P_{3-\phi} = \frac{V_L^2}{R}$$

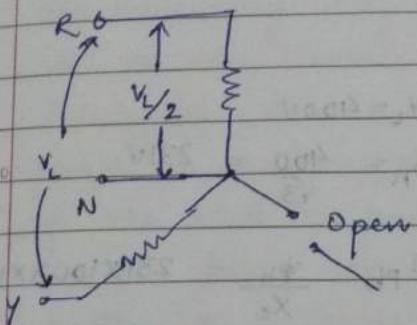

$$\text{Total Power} = \frac{2 \left(\frac{V_L}{2} \right)^2}{R} = \frac{V_L^2}{2R} = P_3$$

$$\% P_{red} = \left(\frac{V_L^2}{R} - \frac{V_L^2}{2R} \right) \times 100 = 50\%$$


$$\frac{V_L^2}{R}$$

ii) 33.33% \rightarrow Ans

Q. 3) 3- $2\mu F$ capacitors are star connected across a 400V, 50Hz 3-phase 3-wire supply.

- Calculate the current in each line.
- If one of the capacitor is open circuited, find line current & p.d. across each of the two capacitors.
- If one of the capacitor is short circuited then calculate the line current.

Sol:-

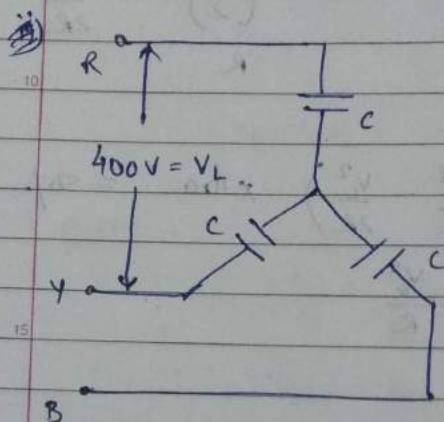


$$i) V_L = 400V$$

$$V_{Ph} = \frac{400}{\sqrt{3}} = 231V$$

$$I_{Ph} = \frac{V_{Ph}}{X_C} = \frac{231 \times 100\pi \times 10^{-6}}{2\pi f C}$$

$$= 1.45A$$

$$I_L = I_{Ph} = 1.45A$$

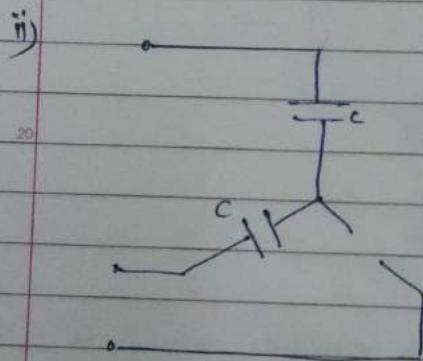


$$\text{Total Capacitance} = \frac{20 \times 20}{20+20}$$

$$= 10\mu F$$

$$X_C = \frac{1}{2\pi f C} = \frac{10^6}{100\pi \times 20}$$

$$= 318.3\Omega$$
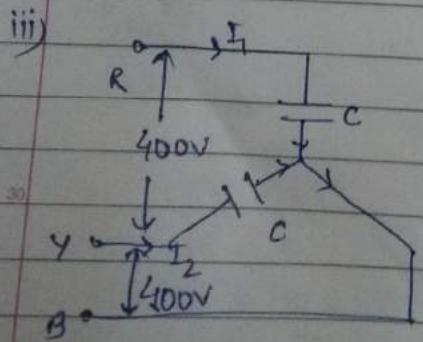
$$I_L = \frac{V_{Ph}}{X_C} = \frac{231 \times 400}{318.3} = 1.21A$$



$$X_C = \frac{1}{2\pi f C} = \frac{10^6}{2\pi \times 50 \times 20} = 159.15\Omega$$

$$I_1 = \frac{V_L}{X_C} = \frac{400}{159.15} = 2.5A$$

$$I_2 = \frac{V_L}{X_C} = \frac{400}{159.15} = 2.5A$$

Camlin	Page
Date	/ /

$$\begin{aligned}
 I_3 &= I_1 + I_2 \quad (\text{vector sum of } I_1 \text{ & } I_2) \\
 &= 2 \times 2.5 \times \cos 30^\circ \\
 &= 5 \times \frac{\sqrt{3}}{2} = 4.33 \text{ A}
 \end{aligned}$$

Power Measurement in Three-Phase Circuits :-


For measuring poly-phase power, we use Blondel's Theorem. Acc. to this theorem, when power is supplied by K-wire A.C. system, the no. of watt meters required to measure the power is one less than the no. of wires (i.e. K-1) regardless of the load is unbalanced or balanced.

Hence, we require 3 watt meter for 3-phase, 4-wire system and 2-watt meters for 3-phase, 3-wire systems.

Two-Watt Meter Method :-

This method is used to measure power in a 3-phase 3-wire star, or delta connected balanced or unbalanced load.

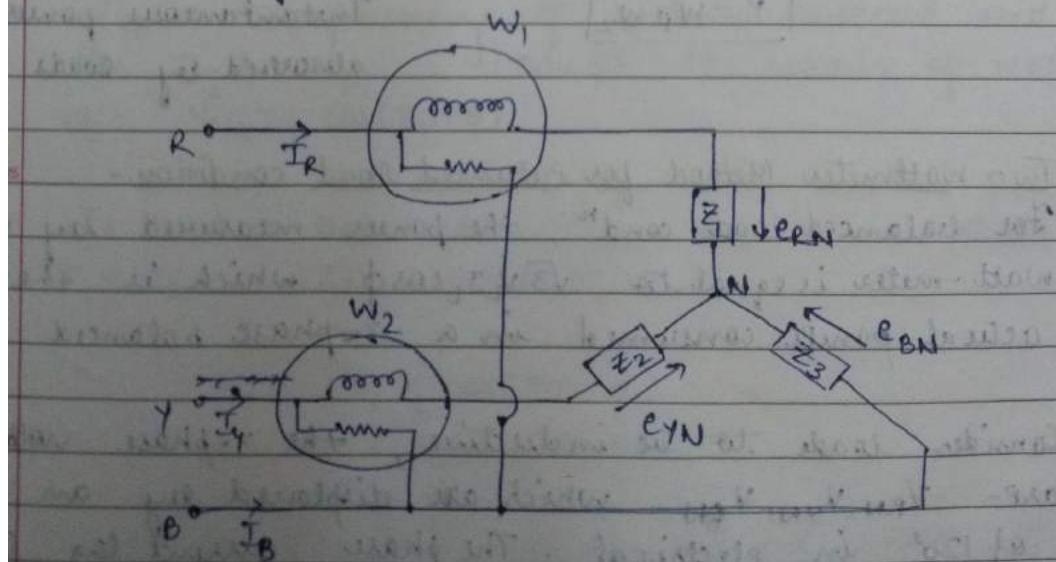In this method, sum of power measured by 2-watt metres i.e. $W_1 + W_2 =$ The total power (instantaneous) absorbed by 3 loads Z_1, Z_2 and Z_3 .



Consider Star Connection

Instantaneous current through current coil of w_1 ,
 $w_1 = I_R$

Instantaneous p.d. across potential coil of w_1 ,
 $e_{RN} - e_{BN}$

Instantaneous power measured by w_1
 $w_1 = (e_{RN} - e_{BN}) I_R$

Similarly for watt meter 2 :

Instantaneous current through current coil of w_2 = I_Y

Instantaneous p.d. across potential coil of w_2
 $e_{YN} - e_{BN}$

Instantaneous power measured by w_2
 $w_2 = I_Y (e_{YN} - e_{BN})$

Now,

$$\begin{aligned} w_1 + w_2 &= I_R (e_{RN} - e_{BN}) + I_Y (e_{YN} - e_{BN}) \\ &= I_R e_{RN} + I_Y e_{YN} - e_{BN} (I_R + I_Y) \\ &= I_R e_{RN} + I_Y e_{YN} + I_B e_{BN} \quad [\because I_R + I_Y + I_B = 0] \end{aligned}$$

$P = w_1 + w_2$

↓
Instantaneous power absorbed by loads


* * * Two Wattmeter Method for balanced load condition:-
For balanced load condn, the power measured by two watt-meter is equal to $\sqrt{3} V_L I_L \cos\phi$ which is the actual power consumed in a 3-phase balanced load.

Consider loads to be inductive, if the 3-phase voltages are V_{RN}, V_{YN}, V_{BN} which are displaced by an angle of 120° in electrical. The phase current lag behind

Pg-703 Table wattmeter reading variation with ϕ .

Comlin	Page
Date	/ /

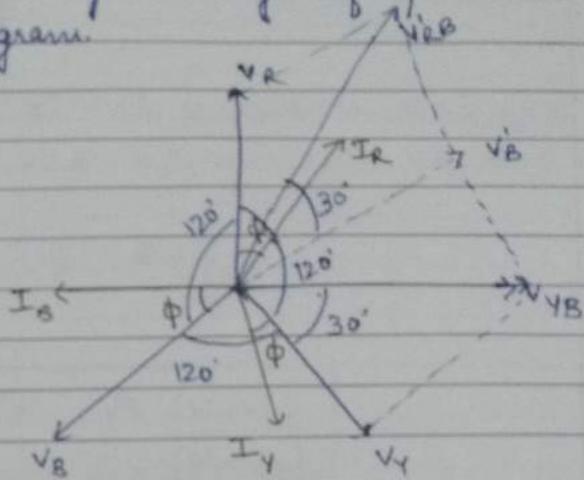Their respective voltages by an angle of ϕ which is shown in phasor diagram.



Current through watt meter $w_1 = I_R$

P.d. across voltage coil of $w_1 \Rightarrow V_{RB} = V_R - V_B$

V_{RB} is compounding of V_R & V_B with a phasor diff. of $(30^\circ - \phi)$ b/w V_{RB} & I_R .

Reading of wattmeter 1 $\Rightarrow w_1 = V_{RB} I_R \cos(30 - \phi)$

Similarly for wattmeter 2 \Rightarrow

Current through wattmeter $w_2 = I_Y$

P.d. across voltage coil of $w_2 \Rightarrow V_{YB} = V_Y - V_B$

V_{YB} is compounding of V_Y & V_B reversed and angle b/w I_Y & V_{YB} $= (30 + \phi)$. So, reading of wattmeter 2

$$w_2 = V_{YB} I_Y \cos(30 + \phi)$$

As load is balanced $V_{RA} = V_{YB} = \text{line voltage } V_L$ and $I_Y = I_R = \text{line current } I_L$

$$\therefore w_1 = V_L I_L \cos(30 - \phi)$$

$$w_2 = V_L I_L \cos(30 + \phi)$$

$$\begin{aligned} \therefore \text{Total power} &= w_1 + w_2 = V_L I_L [\cos(30 - \phi) + \cos(30 + \phi)] \\ &= \sqrt{3} V_L I_L \cos \phi \end{aligned}$$

classmate
Date 2/2/17
Page

Two Wattmeter Method:-

$$W_1 + W_2 = V_L I_L \cos(30^\circ - \phi) + V_L I_L \cos(30^\circ + \phi) = \sqrt{3} V_L I_L \cos \phi \quad \text{--- (1)}$$

$$W_1 - W_2 = V_L I_L \cos(30^\circ - \phi) - V_L I_L \cos(30^\circ + \phi) = V_L I_L \sin \phi \quad \text{--- (2)}$$

Divide eqⁿ (2) by (1)

$$\frac{W_1 - W_2}{W_1 + W_2} = \frac{\sqrt{3} \sin \phi}{\sqrt{3} \cos \phi}$$

$$\tan \phi = \sqrt{3} \frac{(W_1 - W_2)}{(W_1 + W_2)}$$

$$\phi = \tan^{-1} \left[\sqrt{3} \frac{(W_1 - W_2)}{(W_1 + W_2)} \right]$$

Q-1 Phase voltage and current of a star connected inductive load is 150V and 25A. Power factor of load is 0.707 lagging. Assuming that the system is 3-wire and power is measured by using 2 wattmeters, find the readings of wattmeters.

$$V_{ph} = 150V$$

$$V_L = 150\sqrt{3} = 259.807 V$$

$$I_L = P_{ph} = 25A$$

$$\text{Total power} = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 150 \times \sqrt{3} \times 0.707 \times 25 = 450 \times 0.707 \times 25$$

$$W_1 + W_2 = 7954W \quad \text{--- (1)}$$

$$\cos \phi = 0.707$$

$$\phi = \cos^{-1}(0.707)$$


$$\phi = 45^\circ$$

$$\tan \phi = 1$$

$$\tan \phi = \sqrt{3} \frac{(W_1 - W_2)}{(W_1 + W_2)}$$
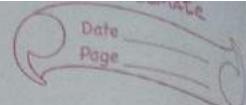
$$1 = \sqrt{3} \frac{(W_1 - W_2)}{7954} \Rightarrow W_1 - W_2 = \frac{7954}{\sqrt{3}} = 4592 \quad \text{--- (2)}$$



Eqⁿ ① + ②

$$2W_1 = 7954 + 4592 = 12546$$

$$W_1 = 6273 \text{ W}$$

$$W_2 = 1681 \text{ W}$$

Q:- ② In a balanced 3-phase 400 V circuit, the line current is 115.5 A, when power is measured by 2-wattmeter method 1 wattmeter reads 40kW & other reads zero. What is the power factor of the load?

If power factor is unity & line current will be same what would be the readings of each wattmeter?

⑥ The degree to which a magnetic field can magnetize a material



CLASSMATE
Date _____
Page _____

unit - III
MAGNETIC CIRCUITS

Some important definitions :-


1. Magnet (Natural, Artificial, Permanent, Temporary)
2. Classification of Magnetic Materials (Para, Ferro, Non, Dia)
3. Magnetic field and its properties
4. Magnetic Induction
5. Magnetic Flux \rightarrow No. of magnetic field lines passing through surface
6. Magnetic Intensity or Magnetising Force (H)
7. Permeability $\rightarrow \mu = B/H$ Measure of ability of material to support magnetic field
8. Relation b/w 'B' & 'H' ($B = \mu H$) the formation of mag. field within
9. Magnetic effect of electric current
10. Magnetic field produced by a Solenoid
11. Electromagnet
12. Magnetic Circuit - closed path followed by magnetic flux
13. MMF (Magneto motive force) - work done in carrying unit magnetic pole once through entire mag. circuit.
14. Reluctance (S) - Opposition offered to the magnetic flux.

$$S = \frac{l}{\alpha \mu_0 H_r}$$

15. Permeance - Reciprocal of reluctance

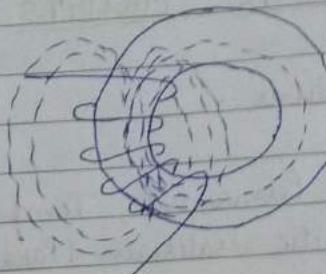16. Leakage flux and fringing :- When a current is passed through the solenoid, magnetic flux is set up. Most of the flux is set up in the core and is called useful flux ' Φ_u '. However some of the flux is just set up around the coil & is not utilized for any useful work. It is called leakage flux ' Φ_l '. So, total flux $\Phi_T = \Phi_u + \Phi_l$.





② Fringing -

when flux is set up in a core which consist of an air gap also. The flux passes through air gap as well and tends to bulge outwards at the interface of air gap. This increases the effective area in the air gap and decreases the flux density. This phenomena is known as fringing. Fringing is directly proportional to length of air gap.

17. Comparison b/w Magnetic & Electrical Circuits

Similarities - path in which ϕ flows from a voltage / current source

- (I) Definition (Electric & Magnetic cts)
- (II) Flux (Magnetic), Current (Electrical)
- (III) ~~W. of MMF that~~ EMF - Electric potential for a source
- (IV) Reluctance, Resistance
- (V) Permeance, Conductance
- (VI) Permeability, Conductivity
- (VII) Reluctivity, Resistivity
- (VIII) Flux density, Current density
- (IX) Magnetic intensity, Electric intensity


$$H = \frac{NI}{l}$$

$$E = \frac{V}{d}$$


<u>Dissimilarities:-</u>	
Magnetic	Electrical
(i) Magnetic flux does not flow but it sets up in the magnetic circuit.	(i) Electric current actually flows in an electric circuit.
(ii) For magnetic flux there is no perfect insulator. It can be even set up even in non-magnetic materials like air, rubber, glass.	(ii) For electric current, there are large no. of perfect insulators like air, glass, rubber.
(iii) The reluctance of a magnetic circuit is not constant rather it varies with the value of B . It is because the value of μ_r changes continuously.	(iii) The resistance of an electric circuit is almost constant as its value depends on the value of j^2 which is almost constant.
(iv) Once the magnetic flux is set up in a magnetic material, no energy is further expended.	(iv) Energy is expended continuously as long as current will flow through the circuit.

Analysis of Magnetic Circuits:-

1) Series Magnetic Circuit :-

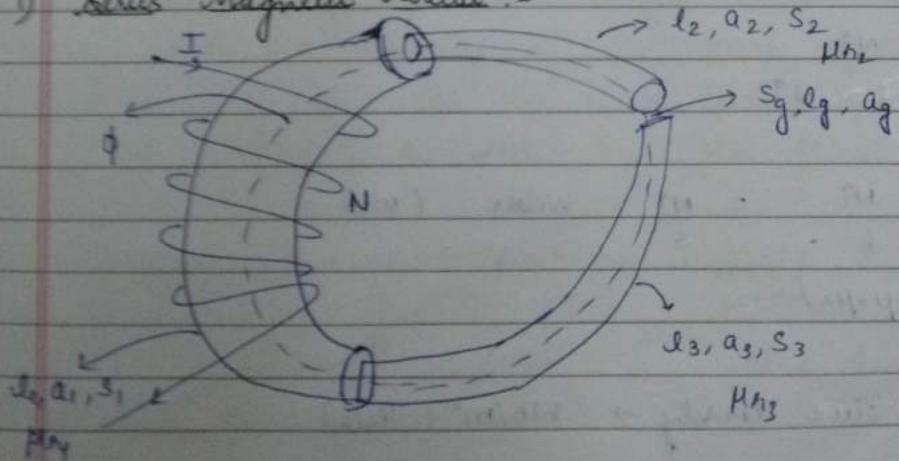

$$\text{Total reluctance} , S = S_1 + S_2 + S_3 + S_g \\ = \frac{l_1}{a_1 \mu_0 \mu_{r1}} + \frac{l_2}{a_2 \mu_0 \mu_{r2}} + \frac{l_3}{a_3 \mu_0 \mu_{r3}} + \frac{l_g}{a_g \mu_0}$$

$$\text{Total MMF} = \Phi \cdot S \\ = \Phi \left[\frac{l_1}{a_1 \mu_0 \mu_{r1}} + \frac{l_2}{a_2 \mu_0 \mu_{r2}} + \frac{l_3}{a_3 \mu_0 \mu_{r3}} + \frac{l_g}{a_g \mu_0} \right]$$

$$\therefore B = \frac{\Phi}{A} \\ = \frac{B_1 l_1}{\mu_0 \mu_{r1}} + \frac{B_2 l_2}{\mu_0 \mu_{r2}} + \frac{B_3 l_3}{\mu_0 \mu_{r3}} + \frac{B_g l_g}{\mu_0}$$

$$\therefore H = \frac{B}{\mu_0 \mu_r}$$

$$\therefore H = H_1 l_1 + H_2 l_2 + H_3 l_3 + H_g l_g$$

Some important formulae:-

1) $H = \frac{NI}{2\pi r}$ ampere turns/metre (AT/m)

2) $H = \frac{\Phi}{A \mu_0 \mu_r}$

3) $H \cdot l = NI$ (According to Work Law)
= Total ampere turns

$$Hl = NI$$

$$\frac{\Phi}{A \mu_0 \mu_r} \cdot l = NI$$

$$\Phi = \frac{NI}{\left(\frac{l}{A \mu_0 \mu_r} \right)} = \frac{NI}{S} \text{ Weber (Wb)}$$

Flux density \rightarrow Wb/m² (Tesla)

Date _____
Page _____

$$q) \phi = \frac{NMF}{\text{Reluctance}}$$

Q-1) Flux density of 0.12 Wb/m^2 is required in the 2mm air gap of an electromagnet having an iron path 1m long. Calculate the magnetising force and current required if the electromagnet has 1273 turns. Assume $(\mu_r)_{Fe} = 1500$.

Sol:-

$$l_g = 2 \text{ mm}, \quad l = 1 \text{ m}, \quad N = 1273, \quad \mu_r = 1500, \quad \frac{\phi}{a} = 0.12 \text{ T}$$

\approx

$$H = H_1 l_1 + H_2 l_2$$

$$= \frac{B}{\mu_0 \mu_r} \cdot l_1 + \frac{B}{\mu_0} \cdot l_2$$

$$= \frac{0.12}{4 \pi \times 10^{-7}} \left[\frac{2 \cdot 1}{1500} + 2 \times 10^{-3} \right]$$

$$= \frac{0.12}{4 \pi \times 10^{-7}} \times 2.67 \times 10^{-3}$$

$$= 254.65$$

$$I = \frac{Hl}{N} = \frac{\text{Total ampere turns}}{N}$$

$$= \frac{254.65}{1273} = 2 \text{ A}$$

Q-2) An iron ring of mean length 1m has an air gap of 1mm & a winding of 200 turns. If the relative permeability of iron is 500 when a current of 1A flows through the coil. Find the flux density.

Sol:-

$$l_g = 1 \text{ mm}, \quad l_T = 1 \text{ m}, \quad N = 200 \text{ turns}, \quad \mu_r = 500, \quad I = 1 \text{ A}, \quad B = ?$$

$$\Phi = \frac{B}{A}$$

$$mmf = \Phi \cdot S$$

$$NI = \Phi \left[\frac{l_1}{a \mu_0 \mu_r} + \frac{l_g}{a \mu_0} \right]$$

CLASSEmate
Date _____
Page _____


$$200 \times 1 = \frac{B\phi}{\mu_0} \left[\frac{0.999}{500} + 10^{-3} \right]$$

$$200 \times 4 \times 10^{-4} = B \left[2.99 \times 10^3 \right]$$

$$B = 0.0847$$

Q-3) A ring has a diameter of 21 cm and a cross sectional area of 10 cm^2 . The ring is made up of semi-circular sections of cast iron & cast steel, with each joint having a reluctance equal to an air gap of 0.2 mm . Find the ampere turns required to produce a flux of 8×10^{-4} . The values of μ_r for cast steel & cast iron are 800 & 166.

Sol:-

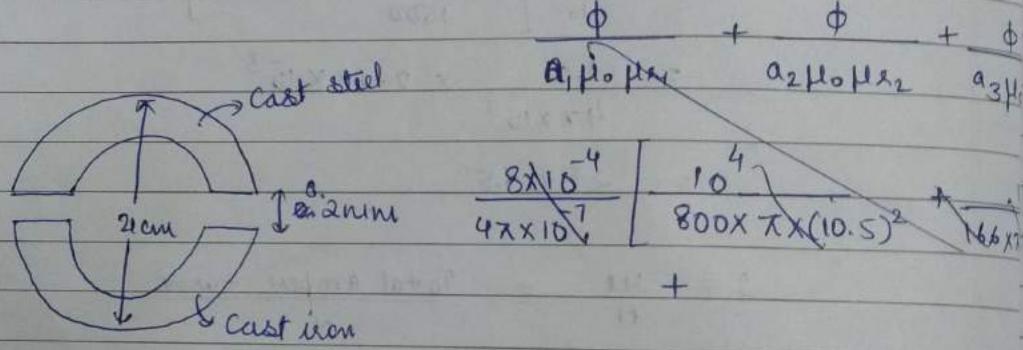

$$\frac{8 \times 10^{-4}}{4 \pi \times 10^{-7} \times 10 \times 10^{-4}} \left[\frac{1}{800} + \frac{1}{166} + 1 \right] = 2 \times 10^6 \left[1.007 \right] = 6.4125 \times 10^5$$

$$l = \frac{\pi D}{2} = \frac{\pi \times 21 \times 10^{-2}}{2} = 0.329 = 0.33 \text{ m}$$

~~$$\begin{aligned} \text{Total ampere turns} &= 0.33 \times 6.4125 \times 10^5 \\ &= 2.116 \times 10^5 \end{aligned}$$~~

Q-4) The ring shaped core as shown in figure is made of a material having relative permeability of 1000. The flux density in the smallest area of cross-section is 2 T. If the current through the coil is not to exceed 1.5 A, compute the no. of turns in the coil.

$$l_1 = 10 \text{ cm}, \quad a_1 = 4 \text{ cm}^2, \quad l_2 = 15 \text{ cm}, \quad a_2 = 3 \text{ cm}^2, \quad l_3 = 20 \text{ cm}, \quad a_3 = ?$$

Sol:-

$$\phi s = NI$$

$$, \mu_r = 1000$$

$$\phi = B \times A$$

$$I = 1.5 \text{ A}$$

$$S = S_1 + S_2 + S_3$$

$$= \frac{1}{\mu_0 \mu_r} \left[\frac{l_1}{a_1} + \frac{l_2}{a_2} + \frac{l_3}{a_3} \right]$$

$$= \frac{1}{4\pi \times 10^{-7} \times 1000} \left[\frac{10 \times 10^{-2}}{4 \times 10^{-4} \times 10^{-2}} + \frac{15 \times 10^{-2}}{3 \times 10^{-4}} + \frac{20 \times 10^{-2}}{2 \times 10^{-4}} \right]$$

$$= \frac{10^4}{4\pi} \left[\frac{250}{4} + \frac{1500}{3} + \frac{1000}{2} \right]$$

$$= \frac{10^4}{4\pi} \times 1750$$

$$= 1.393 \times 10^6$$

Q(5) An iron ring has a cross-section of 3cm^2 and circumference of 25cm . An air gap of 0.4mm has been cut across the section of the ring. The ring is wound with a coil of 200 turns through which a current of 2A is passed. If the total magnetic flux is 0.24mWb , Find the relative permeability of iron.

Sol:-

$$D = 25\text{cm}, \quad a = 3\text{cm}^2, \quad l_g = 0.4\text{mm}, \quad N = 200, \quad I = 2\text{A}, \quad \phi = 0.24\text{mWb}$$

$$M_A = \frac{\phi}{H_0 \mu_R} \quad H \cdot l = N \cdot I$$

$$H_1 l_1 + H_2 l_2 = N \cdot I$$

$$\frac{B_1 l_1}{H_0 \mu_R} + \frac{B_2 l_2}{H_0} = N \cdot I$$

$$\frac{\phi l_1}{a \mu_0 \mu_R} + \frac{\phi l_2}{a \mu_0} = N \cdot I$$

$$\frac{0.24 \times 25 \times 10^{-8}}{3 \times 10^{-2} \times 10^{-6}} + \frac{\phi}{a \mu_0} \left[\frac{l_1}{\mu_R} + \frac{l_2}{\mu_0} \right] = N \cdot I$$

$$200 \times 2 = \frac{0.24 \times 10^{-3}}{3 \times 10^4 \times 4 \pi \times 10^{-7}} \left[\frac{25 \times 10^{-2}}{2 \mu} + 0.4 \times 10^{-3} \right]$$

$$400 = \frac{24 \times 10^{-8}}{12 \pi \times 10^{-6} \mu} \left[0.393 + 0.4 \times 10^{-4} \right]$$

~~$$400 = \frac{0.24 \times 10^{-3}}{10^{-6}} \times \frac{2 \times 10^{-4}}{\mu} = 0.393 + 4 \times 10^{-4}$$~~

~~$$\frac{0.24 \times 10^{-3}}{10^{-6} \mu} = 0.393 + 4 \times 10^{-4}$$~~


~~$$200 \times 10^{-6} - 4 \times 10^{-4} = \frac{0.393}{\mu} + \frac{4 \times 10^{-4}}{10^{-4} \times 2.283}$$~~

~~$$\mu = \frac{10^4 \times 0.393}{2.283} = 1721.4$$~~

~~$$4 \times 2.283 \times 10^{-4} = \frac{1}{\mu}$$~~

$$\mu = 1095$$

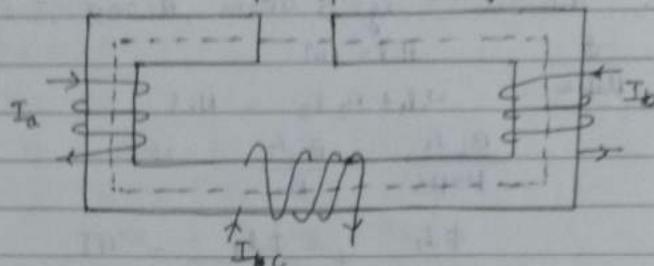Q-6) A rectangular iron core shown in figure. It has mean length of magnetic path of 100 cm. Cross section of armature $\mu_r = 1400$ and air gap of 5 mm cut in the core. The 3 coils carried by the core have no. of turns $N_a = 335$, $N_b = 600$, $N_c = 600$ and their respective currents are 1.6, 4 and 3. The direction of currents are shown in figure. Find the flux in the air gap.



Ans:-

$$\text{mmf} = \phi \cdot S$$

$$\phi = \frac{\text{mmf}}{S}$$

$$\begin{aligned} \text{① total mmf} &= N_a I_a + N_b I_b + N_c I_c \\ &= 335 \times 1.6 + 600 [4 - 3] \\ &\quad 536 + 600 = 1136 \end{aligned}$$

$$S = S_1 + S_2$$

$$= \frac{l_1}{\mu_0 \mu_r} + \frac{l_2}{\mu_0} = \left[\frac{100 \times 10^{-2}}{1400} + \frac{5 \times 10^{-3}}{1} \right] \frac{1}{\mu_0}$$

$$l_1 = 100 - 0.5$$

$$= \left[\frac{1}{1400} + 0.005 \right] \frac{10^7}{4 \pi \times 10^{-4} \times 4}$$

$$= \frac{5.714 \times 10^8}{4 \times 16 \pi} = -0.4547 \times 10^4$$

$$\phi = \frac{1136}{4547} = 0.2498 = 1.136 \times 10^7 \text{ AT/BS}$$

$$\phi = \frac{1136}{1136 \times 10^4} = 10^{-4} \text{ Wb}$$

1.6 Excitation in Magnetic Circuits:-

Electromagnetic Induction
 - Induced emf → statically
 - → dynamically

Expressions for Self Inductance:-

$$1) e = L \frac{dI}{dt} \Rightarrow L = \frac{e}{dI/dt}$$

$$2) L = \frac{N\Phi}{I}$$

$$3) L = \frac{N^2}{S}$$

Expressions for mutual Inductance :-

$$1) e_m = M \frac{dI_1}{dt}$$

$$M = \frac{e_m}{dI_1/dt}$$

$$2) M = \frac{N_2 \Phi_2}{I_1}$$

$$3) M = \frac{N_1 N_2}{S}$$

Q-1) Calculate inductance of a toroid 25cm mean diameter & 6.25 cm² circular cross-section wound uniformly with 1000 turns of wire. Hence, calculate the emf induced when current in it increases at the rate of 100 A/s.

Soln:-

$$N = 1000, \frac{dI}{dt} = 100, a = 6.25 \text{ cm}^2, D = 25 \text{ cm.}$$

$$\therefore L = \frac{N^2}{S}$$

BL Manerja Vol. I Pg - 303

Ex:- 7.18, 7.19

A few of
0.5 mwb
900 turns

$$S = \frac{l}{\alpha \mu_0 A} = \frac{7 \times 25 \times 10^2}{0.4 \times 1.27 \times 10^{-6} \times 1 \times 6.25 \times 10^{-4}} = \frac{10^9}{12.8}$$


$$L = \frac{10^6}{10^9} = 10^{-3}$$

$$e = 0.1 \text{ V}$$

Coefficient of Coupling :-

The fraction of magnetic flux produced by the current in one coil that links with the other is known as coefficient of coupling b/w the two coils denoted by 'k'.

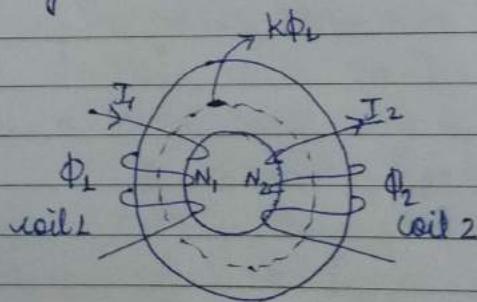If the flux produced by one coil is completely linked with other, then the value of 'k' is '1' and coils are said to be magnetically tightly coupled whereas if the flux produced by one coil does not link with the other, then the value of 'k' is '0' & the coils are said to be magnetically isolated.



Consider a magnetic ckt. in which 2 coils are present coil-1 & 2. Let current I_1 flows through the coil 1, then

$$L_1 = \frac{N_1 \Phi_1}{I_1}$$

$$\text{and } M = \frac{N_2 \Phi_{12}}{I_1} = \frac{N_2 k \Phi_1}{I_1} \quad \text{--- (1)}$$

Camlin	Page
Date	/ /

Similarly for coil 2, $L_2 = \frac{N_2 \phi_2}{I_2}$

$$M = \frac{N_1 \phi_{21}}{I_2} = \frac{N_1 K \phi_2}{I_2} \quad \text{--- (2)}$$

Now, multiply eqⁿ ① & ②

$$M^2 = \frac{N_1 N_2 K^2 \phi_1 \phi_2}{I_1 I_2} = K^2 L_1 L_2$$

$$M = K \sqrt{L_1 L_2}$$

$$\boxed{K = \frac{M}{\sqrt{L_1 L_2}}}$$

Q.1) Two identical 750 turns coils A & B lie in a parallel planes. A current changing at the rate of 1500 A/s in A induces an emf of 11.25 V in B. Calculate the mutual inductance of the arrangement if the self inductance of each coil is 15 mH . Calculate flux produced in coil A (per Amp.) & the % of this flux which links with the turns of B.

Sol:-

~~$$M = \frac{e}{\frac{di}{dt}} = \frac{dAIXdt}{dt} \quad \frac{dI_A}{dt} = 1500$$~~

$$e = M \frac{dI_A}{dt}$$

$$11.25 = M \times 1500$$

$$M = 7.5 \times 10^{-3} = 7.5 \text{ mH}$$

$$\begin{aligned} \phi_{12} &= \frac{MI_1}{N_2} \\ &= 7.5 \times 10^{-3} \end{aligned}$$

$$I_1 = \frac{N_1 \phi_1}{I_1}$$

$$\begin{aligned} \frac{\phi_1}{I_1} (\text{Flux per amp.}) &= \frac{15 \times 10^{-3}}{750} \\ &= 2 \times 10^{-5} \text{ Wb/A} \end{aligned}$$

Comlin Page
Date / /

$$K = \frac{M}{\sqrt{L_2}}$$

$$= \frac{M}{\sqrt{L^2}} = \frac{M}{L} = \frac{I_1 S}{15} = 50\%$$


~~H.W Q-2)~~ Two coils A of 12500 turns and B of 16000 turns lie in parallel planes so that 60% of the flux produced in A links with B. It is found that a current of 5A in A produces a flux of 0.6 mWb while the same current in B produces 0.8 mWb. Determine

- mutual inductance
- coupling coefficient

[Ans. i) $M = 1.15 H$, ii) $K = 0.586$]

Magnetic Hysteresis and B-H curve:- or Hysteresis loop

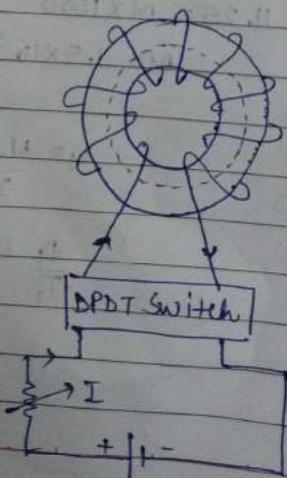when a magnetic material is magnetised first in one direction then in another, it is found that magnetic flux density B in the material lags behind the applied magnetising force ' H '. This phenomena of lagging is known as magnetic hysteresis.




DPDT: Double Pole
Double Throw

Comlin	Page
Date	/ /

Consider a magnetic material on which a solenoid is wound uniformly. The solenoid is connected to a d.c. source through a D.P.T switch.

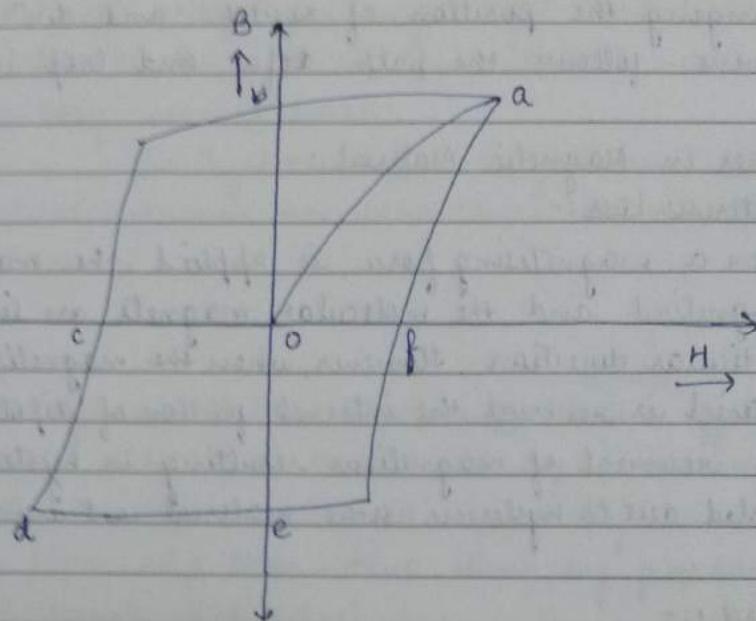When the field intensity H is increased gradually by increasing current in the solenoid, the flux density B also increases until a saturation point a is reached.



If now the magnetising force is gradually reduced to zero the flux density does not become zero. This phenomena is known as Residual Magnetism & Retentivity.

Residual Magnetism & Retentivity:-

The value of flux density ob retained by magnetic material is called residual magnetism & the power of retaining this residual magnetism is called retentivity of the material.

To demagnetise the magnetic ring, the H is reversed by reversing the dirⁿ of current. When H is increased in the reverse dirⁿ, the flux density starts decreasing & becomes zero at point c.

✓
 Camlin Page
 Date / /
 Concise Force :-
 The value of magnetising force or required to wipe off the residual magnetism is called coercive force.
 To complete the loop, the magnetising force H increased further in reverse dirⁿ till saturation pt. reaches. Again H is increased in the (+)ve dirⁿ by changing the position of switch and dirⁿ of current. The curve follows the path defa and loop is completed.
 Losses in Magnetic Material :-
 1) Hysteresis Loss :-
 When a magnetising force is applied, the magnetic material is magnetised and the molecular magnets are lined up in a particular direction. However, when the magnetising force in the material is reversed the internal friction of dipole (MM) opposes the reversal of magnetism resulting in hysteresis and energy wasted due to hysteresis in the material is known as hysteresis loss.
 Remedy :-
 This type of losses can be minimized by using suitable magnetic material such as silicon, steel.
 Formula - $P_h = [\eta B_{max}^{1.6} f V] \text{ Watts}$
 where, P_h = Hysteresis loss in Watts
 η = Hysteresis or Steinmetz's constant (in Joule/m^3)
 (Value depends on nature of material)
 f = Frequency of reversal
 V = Volume (material) where magnetic field of magnetic material

2) Eddy Current:-

When a magnetic material is subjected to a changing magnetic field and EMF is induced in the magnetic field material by Faraday's law. Since, the magnetic material is also conducting material, this EMF circulates current within the body of the material. These currents are known as Eddy currents as these currents are not utilized for any useful work. This current produces heat = $I^2 R$, losses Δ in the material which are also known as Eddy current losses.

The hysteresis and eddy current losses in a material are also known as iron losses or core losses or magnetic losses.

Remedy:-

To reduce eddy current loss, we have to reduce effective resistance of the material, which can be reduced by increasing the effective area. This can be achieved by slicing the sheet steel into small pieces and laminating them by fine layers of insulation (varnish, oxide film).

Formula:-

$$[P_e = k_e B_{max}^2 \cdot t^2 f^2] \text{ watts}$$

where, P_e = Eddy current loss (in watts)

k_e = coefficient of eddy current (depends on types of material)

B_{max} = Maximum value of flux density

f = Frequency of reversal of magnetic field

t = Thickness of lamination

To minimize such losses we can decrease eddy current by increasing the resistance of the material by reducing the effective area.

Unit - 4
TRANSFORMERS


Comlin Page
Date / /

Transformer:-

It is static device which transfers A.C. electrical power from one circuit to another without change in frequency but voltage levels are changed.

Working Principle:-

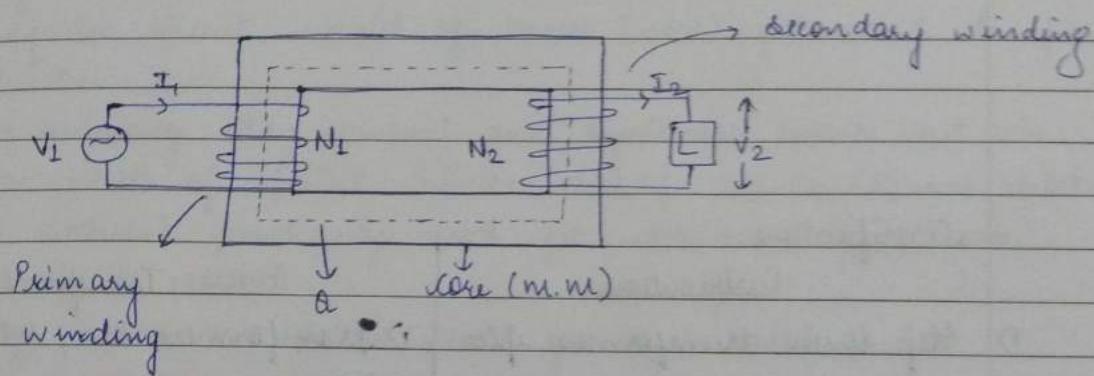It works on phenomena of mutual induction.



Classification:-	
Distribution	Power Transformer
1) Step down transformer upto 500 KVA (kilo volt ampere).	1) Transformers are rated above 500.
2) Generally used for distribution and step down 11 KV into 3 phase 440 V.	2) These are generally used for stepping up and stepping down.
3) Minimum rating is 5 kV.	3) This transformer are operated during load periods only & can be disconnected during light load.
4) These are energised for whole day (24 hrs).	4) Power transformer should have max. efficiency of 80%.
5) This transformer are used generally for varying load throughout the day.	

- 6) Due to this varying load, copper losses are different throughout the day.

- 7) Due to varying copper loss, max^m efficiency is nearly about 50% of full load.

Construction of Transformers :-

- 1) Magnetic circuit:-

- ii) Magnetic circuit consist of linsler (core), yoke and damping structures.

- iii) For reducing Eddy current and hysteresis losses, we use thin sheets of special silicon steel of 0.3 to 0.35 mm thickness.

- (iii) The material practically used for cores and yokes are CRGO and HRGO.

Silicon Steel [C.R.G.O :- Cold Rolled grain oriented
H.R.G.O :- Hot Rolled grain oriented

- (iv) Steel used, should possess high permeability, high resistivity & low coercive force.

- ## 2) Electric circuit:-

In this primary and secondary windings are considered

usually made up of copper. (Nowadays, aluminium wires are used instead of copper).

- ### 3) Dielectric circuit:-

- (ii) The dielectric circuit consist of insulation used at different places in the transformer to insulate the conducting parts.

- (ii) The insulation b/w core & low voltage winding is provided by


an insulation cylinder of paper, bakelite, press board.

(iii) oil ducts are always provided for cooling purpose.

→ Tank & Accessories :-

* Conservative Tank -

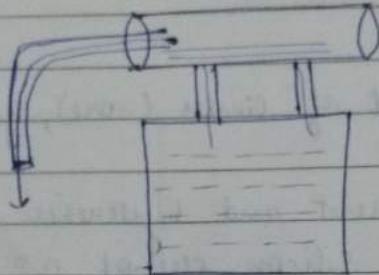The tank is generally used for maintaining oil level in transformer during different weather conditions.




* Breather -

Breather is used for absorbing / extracting moisture from air which is mounted nearly transformer tank.

Silica gel & calcium chlorides are used for absorbing moist.

* Bushings :-

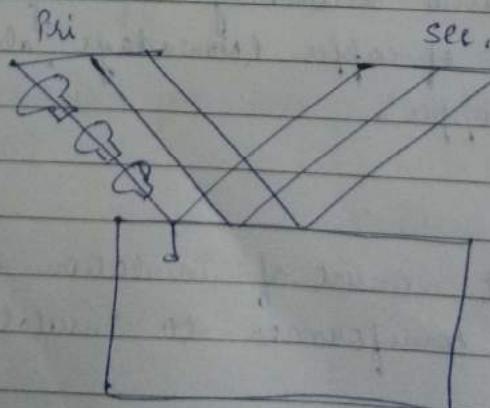Bushings are nothing but simply terminal connections of the winding which are taken out and mounted with insulators.



Camlin	Page
Date	/ /

On Ideal Transformer

- 1) The core of transformer is highly permeable so that it requires very small mmf to set up flux in the core.
- 2) Its leakage flux is zero, i.e. entire flux is confined to the core and links with both the windings.
- 3) Resistance of primary & secondary windings are negligible.
- 4) The losses in the transformer are zero.

EMF Equation of Transformer:-

when alternating voltage is applied to the primary side, it takes a magnetizing current and a flux ' ϕ ' is established in the core. The flux is uniformly distributed in the core & links with all the turns of both the windings. As flux ' ϕ ' is of alternating nature so, due to Faraday's law of EMF, an EMF is induced in primary winding which is given by

$$e_p = -N_p \frac{d\phi}{dt} \quad \text{--- (1)}$$

The main flux ' ϕ ' can be expressed as-

$$\phi = \phi_m \cos \omega t$$

put this value of ϕ in eqⁿ (1)

$$e_p = -N_p \frac{d}{dt} (\phi_m \cos \omega t)$$

$$e_p = N_p \phi_m \omega \sin \omega t$$

The induced emf ' e_p ' will be max. when $\sin \omega t = 1$.

$$\therefore \sin \omega t = 1$$

$$\therefore (e_p)_{\max.} = N_p \omega \phi$$

The RMS value of induced emf in the primary side

$$(E_p)_{\text{rms}} = \frac{E_{\text{max}}}{\sqrt{2}}$$

$$= \frac{N_p W \phi_m}{\sqrt{2}}$$

$$= \frac{2\pi f N_p \phi_m}{\sqrt{2}}$$

$$E_{\text{rms}} = 4.44 f \phi_m N_p$$

Similarly, for secondary winding,

$$E_{\text{rms}} = 4.44 f \phi_m N_s$$

Transformation Ratio :-

$N_p I_p$ For an ideal transformer,

$$N_p I_p = N_s I_s$$

$$V_p I_p = V_s I_s$$

From above eqn's

$$\frac{E_p}{E_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p} = \frac{V_p}{V_s} = k \rightarrow \text{Transformation Ratio}$$

Q-1) A single phase transformer has 350 primary & 1050 secondary turns. Net cross-sectional area of core is 55 cm^2 . The primary winding is connected to 400V, 50Hz single phase supply. Calculate

- (i) Maxm value of flux density in core.
- (ii) Voltage induced in secondary winding.

Sol:-

$\therefore E_p = 4.44 N_p \phi_m f$


$$400 = 4.44 \times 350 \times R_m \times A_i \times 50$$

$$R_m = 0.937$$

$$N_p = 350, N_s = 1050$$

ELECTRICAL ENGINEERING [TS]

CREDIT TO ASHISH JAIN

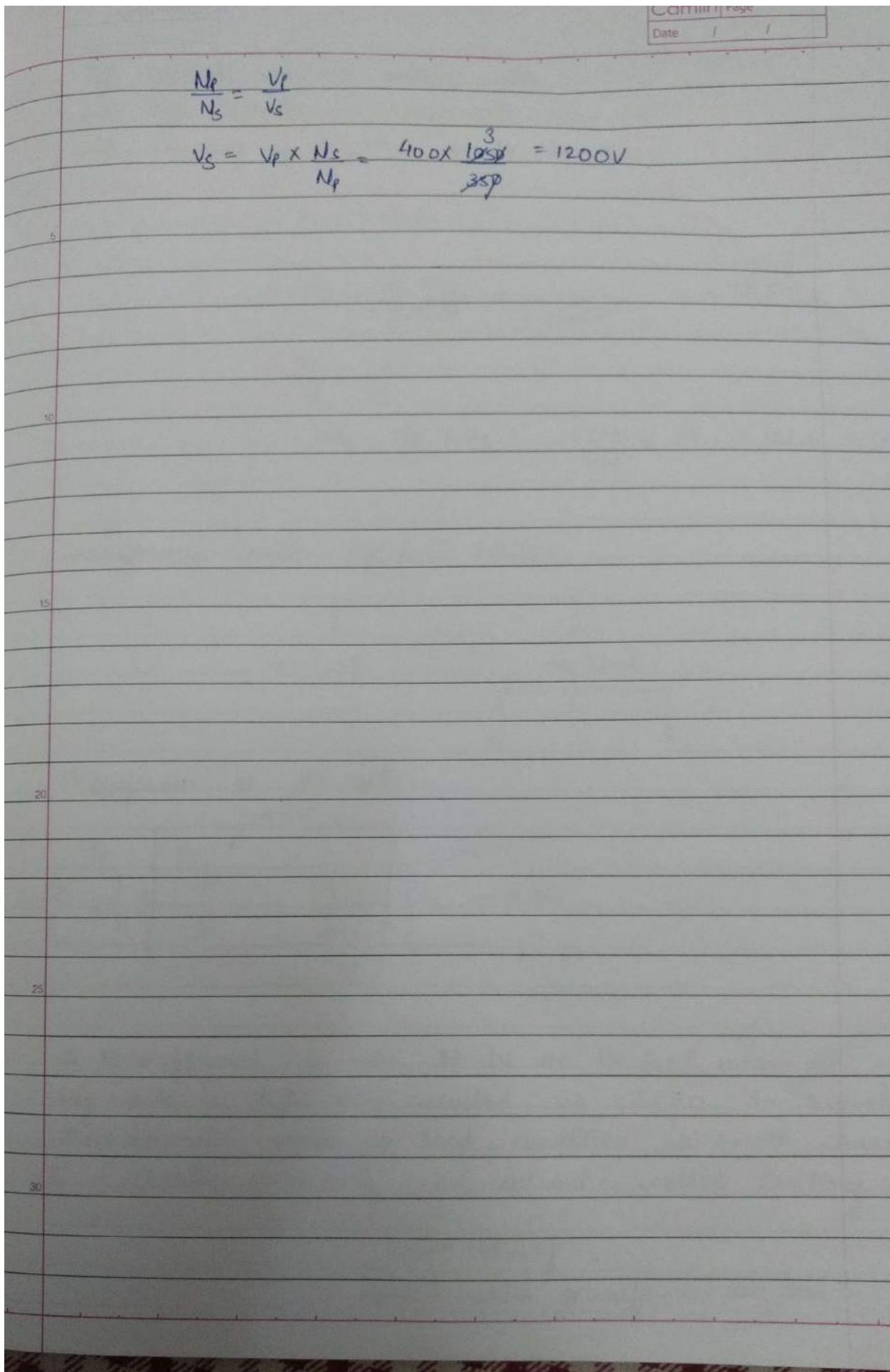

Q:- The required no load voltage ratio in a single phase 50 Hz core type transformer is 6600 volts. Find the no of turns in each winding if the flux is to be 0.06 wb.

$$\frac{6600}{500} = \frac{V_p}{V_s} = \frac{E_s}{E_p}$$

Sol:-


$$E_s = 4.44 N_s \phi_{mef}$$

$$N_s = \frac{6600}{4.44} \times \frac{1}{0.06 \times 50} = 39.5 \approx 38$$


$$\frac{N_p}{N_s} = \frac{V_p}{V_s}$$

$$N_p = \frac{V_p}{V_s} \times N_s = \frac{6600}{500} \times 38 = 501.6 \approx 502$$

Transformer under different loads :-

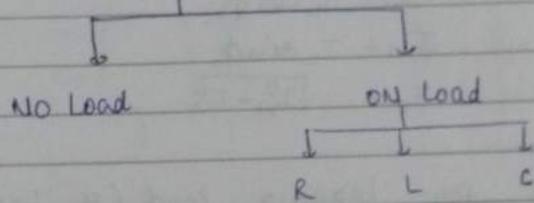

Transformer at NO Load:-

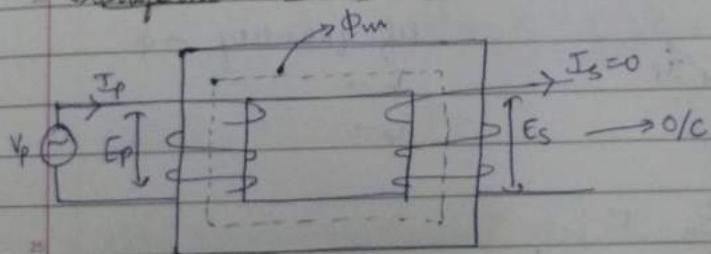


A transformer is said to be on NO load, when its secondary side is left open-circuited i.e. $I_s = 0$. In actual transformer under no load condition, a small current I_0 (usually 2-10% of rated current) called exciting current flows.

Max^m value of current which transformer can bear



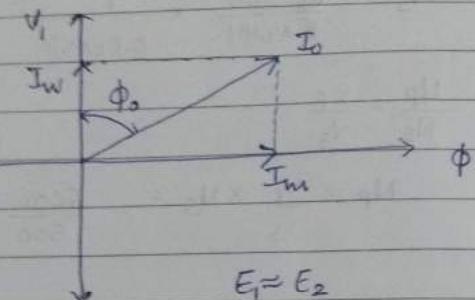is drawn by the primary from the supply. This current has to supply iron or core losses and small amount of copper losses in primary. As I_0 is very small, the copper losses are neglected as compared to core losses. Therefore current lags behind the voltage V_1 by an angle ϕ .





$$I_{w1} = I_0 \cos \phi,$$

$$I_{m1} = I_0 \sin \phi,$$


$$I_0 = \sqrt{I_{w1}^2 + I_{m1}^2}$$

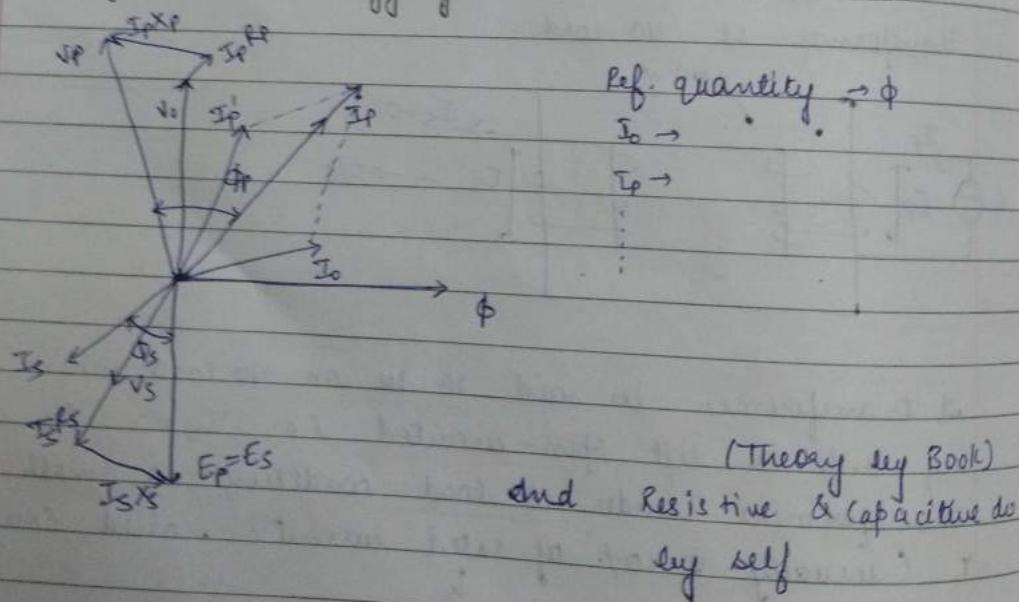Transformer on lagging load (or Inductive Load):-



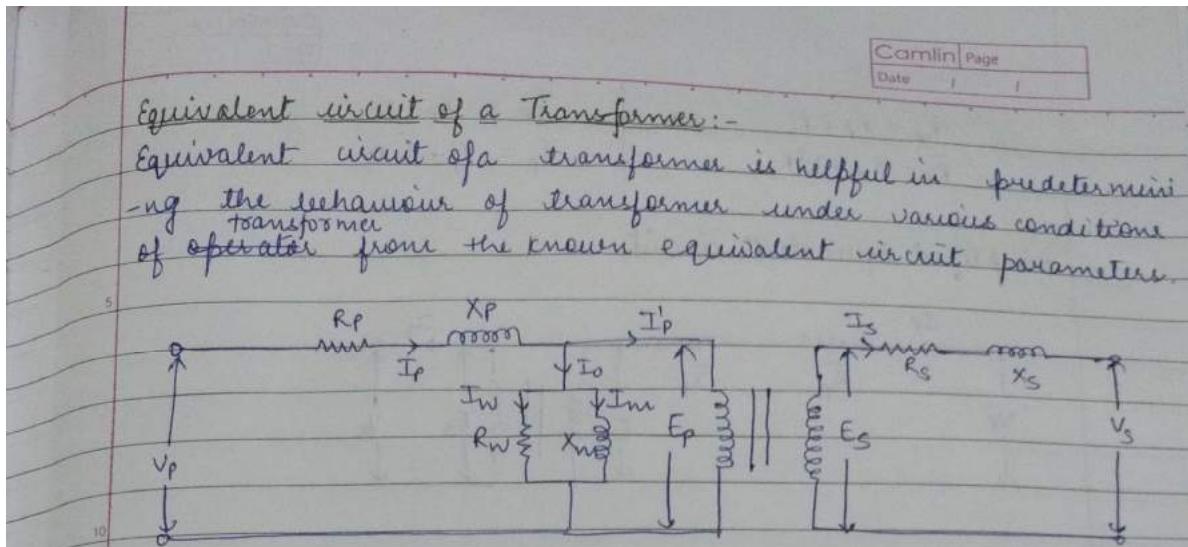

(I) Refer to Primary:-

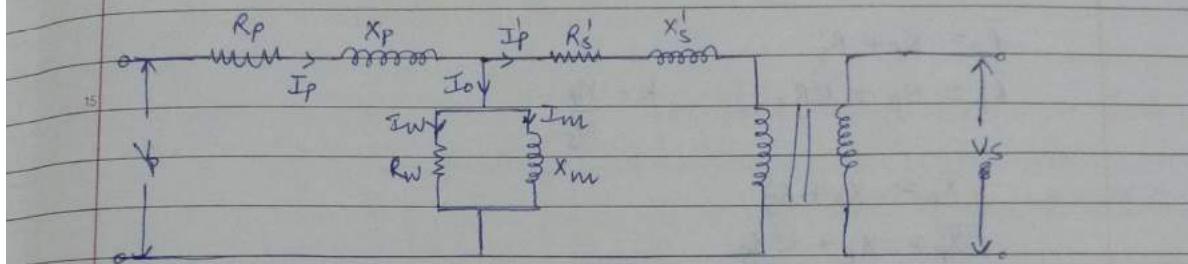


$$(I_p')^2 R'_s = (I_s)^2 R_s$$

$$\therefore R'_s = \left(\frac{I_s}{I_p'}\right)^2 R_s = \left(\frac{N_p}{N_s}\right)^2 R_s = k^2 R_s$$

Similarly, $X'_s = k^2 X_s$

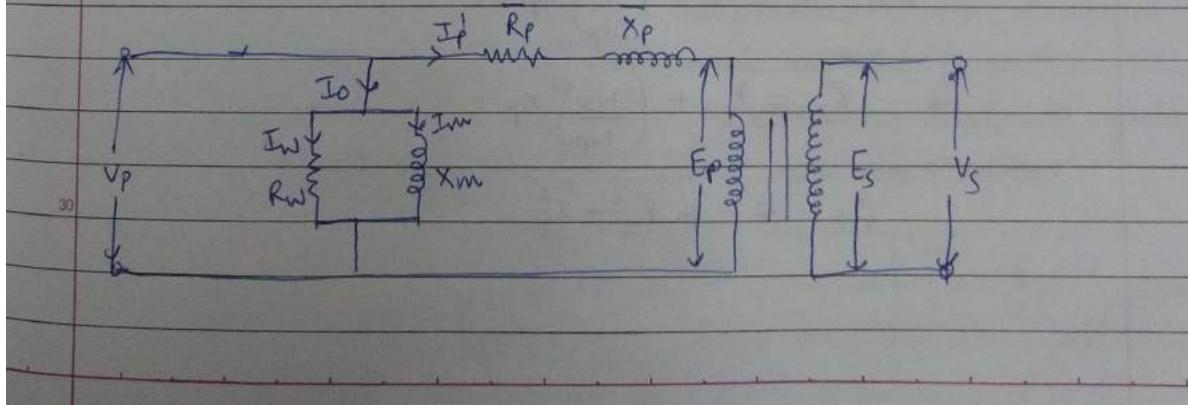Approximate Equivalent circuit refer to 1°:-




$$\bar{R}_p = R_p + R_s'$$

$$\bar{R}_p = R_p + k^2 R_s$$

$$\bar{X}_p = X_p + X_s$$

$$\bar{X}_p = X_p + k^2 X_s$$

Simplified equivalent circuit :-

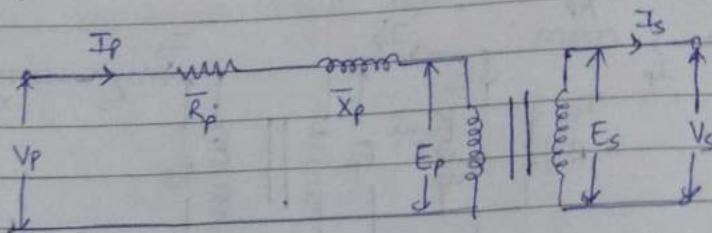

Equivalent Resistance & Reactance :-
(Refer to 1°)

$$\bar{R}_p = R_p + R_s'$$

$$\bar{R}_p = R_p + k^2 R_s, \quad k = \frac{N_p}{N_s}$$

$$\bar{X}_p = X_p + X_s'$$

$$\bar{X}_p = X_p + k^2 X_s$$

Total impedance refer to 1° :

$$\bar{Z}_p = \sqrt{\bar{X}_p^2 + \bar{R}_p^2}$$

Refer to 2°

$$\bar{R}_s = R_s + \frac{R_s'}{k^2 R_p}, \quad k = \frac{N_s}{N_p}$$

$$\text{or } \bar{R}_s = R_s + \left(\frac{N_s}{N_p}\right)^2 R_p$$

$$\& \quad \bar{X}_s = X_s + \left(\frac{N_s}{N_p}\right)^2 X_p$$

$$\therefore Z = \sqrt{\bar{R}_s^2 + \bar{X}_s^2}$$

:-) A 25 kVA, 2200 by 220V, 50Hz single phase transformer, has the following R & leakage reactance

$$R_p = 0.8 \Omega, X_p = 3.2 \Omega$$

$$R_s = 0.009 \Omega, X_s = 0.03 \Omega$$

calculate:-

(i) Equivalent resistance refer 1°

(ii) Equivalent reactance refer 1°

(iii) Equivalent resistance refer 2°

(iv) Equivalent reactance refer 2°.

Sol:-

$$\therefore \frac{E_p}{E_s} = \frac{V_p}{V_s} = \frac{2200}{220} = 10 = \frac{N_p}{N_s}$$

$$f = 50 \text{ Hz}$$

$$\begin{aligned} \text{(i)} \quad \bar{R}_p &= R_p + k^2 R_s \\ &= 0.8 + 100 \times 0.009 \\ &= 0.8 + 0.9 \\ &= 1.7 \Omega \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad \bar{R}_s &= R_s + \frac{1}{100} \times R_p \\ &= 0.009 + \frac{0.8}{100} = 0.017 \Omega \end{aligned}$$

$$\begin{aligned} \text{(iii)} \quad \bar{X}_p &= X_p + k^2 X_s \\ &= 3.2 + 100 \times 0.03 \\ &= 3.2 + 3 \\ &= 6.2 \Omega \end{aligned}$$

$$\begin{aligned} \text{(iv)} \quad \bar{X}_s &= X_s + \frac{1}{100} \times X_p \\ &= 0.03 + \frac{3.2}{100} = 0.062 \Omega \end{aligned}$$

Voltage Regulation :-

The secondary terminal voltage changes with the change in load so, voltage regulation of a transformer is defined as the net change in the 2° terminal voltage from no load to full load expressed as 'a %' of its rated voltage for the 1° voltage.

$$\% \text{ V.R.} = \left(\frac{V_{SNL} - V_{SFLL}}{V_{SFLL}} \right) \times 100$$

| NL : No load.

| FL : Full load

$$\text{Also, } \% \text{VR} = \frac{I_s(\bar{R}_s \cos\phi + \bar{X}_s \sin\phi)}{V_s} \times 100$$

- + → lagging power factor / i.e. inductive load
- → leading power factor / i.e. capacitive load

Q-1) A 2kVA, 400 by 200 V, 50Hz single phase transformer has following parameters as refer to 1' side -

$$\bar{R}_p = 3.2, \bar{X}_p = 4.2$$

Determine the regulation of transformer when operating at full primary current supply

- (i) full load with 0.8 pf lagging,
- (ii) full load with 0.8 pf leading,
- (iii) half load with 0.8 pf lagging

↓
half primary current supply.

Sol:-

$$k = \frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{400}{200} = 2$$

$$\cos\phi = 0.8$$

$$\therefore \sin\phi = \sqrt{1-0.64} = \sqrt{0.36} = 0.6$$

? Refer to 1' :-

$$\therefore \% \text{VR} = \frac{I_p(\bar{R}_p \cos\phi \pm \bar{X}_p \sin\phi)}{V_p} \times 100$$


$$\therefore \text{Current, } I_p = \frac{2000 \text{ A}}{400 \text{ V}} = 5 \text{ A}$$

$$\therefore (\text{i}) \% \text{VR} = 5 \left(\frac{3 \times 0.8 + 4 \times 0.6}{400} \right) \times 100$$

$$= \frac{5(2.4 + 2.4)}{4} = \frac{5 \times 4.8}{4} = 6\%$$

$$(\text{ii}) \% \text{VR} = 0$$
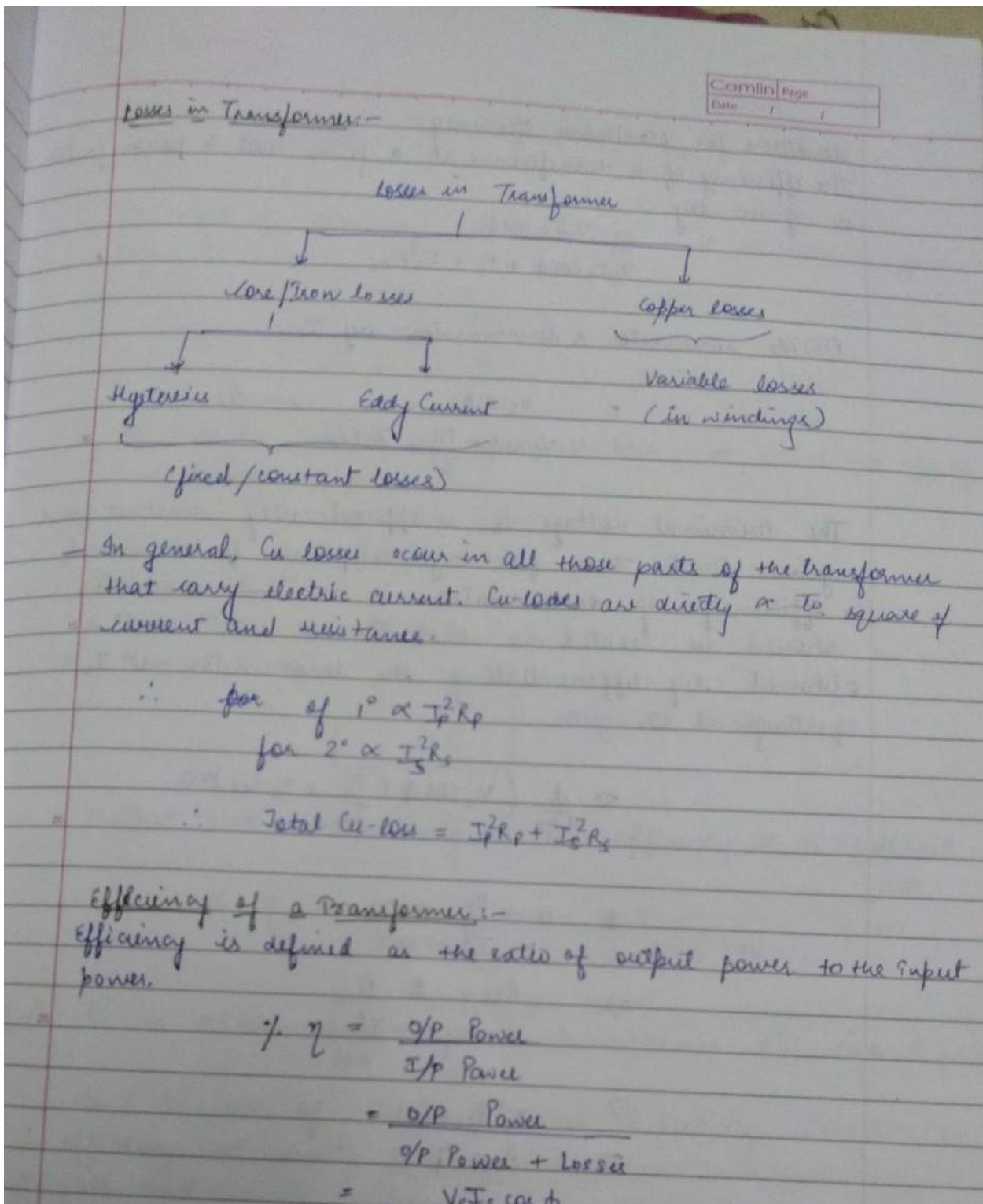
$$(\text{iii}) \% \text{VR} = \frac{5}{2} \left(\frac{2.4 + 2.4}{400} \right) \times 100 = -3\%$$



Condition for Maximum efficiency:-
 The efficiency of a transformer at a given load & power factor
 is given by :-

$$\frac{V_s I_s \cos \phi}{V_s I_s \cos \phi + P_i + I_s^2 R_{\text{es}}}$$

Divide numerator & denominator by I_s

$$= \frac{V_s \cos \phi}{V_s \cos \phi + \frac{P_i}{I_s} + I_s R_{\text{es}}} \quad \text{--- (1)}$$

The terminal voltage V_s is approximately constant for given load. Thus, for a given power factor in load, the efficiency is denominator is min^m & numerator should be treated as constant. So, max^m cond is obtained by differentiating the denominator w.r.t I_s & equating it to zero.

$$\Rightarrow \frac{d}{d I_s} \left(V_s \cos \phi + \frac{P_i}{I_s} + I_s R_{\text{es}} \right) = 0$$

$$\Rightarrow 0 - \frac{P_i}{I_s^2} + R_{\text{es}} = 0$$

$$\Rightarrow R_{\text{es}} = \frac{P_i}{I_s^2}$$

$$\Rightarrow I_s^2 R_{\text{es}} = P_i$$

$$\Rightarrow P_e = P_i$$

Thus, eff of transformer will be max when both the losses are equal.

Camlin Page
Date / /

$$\% \eta_{\max} = \frac{V_s I_s \cos \phi}{(V_s I_s \cos \phi + 2P_i)} \times 100$$

The value of secondary at which eff. will be max is given by:-

$$I_s^2 R_{\text{es}} = P_i$$

$$I_s = \sqrt{\frac{P_i}{R_{\text{es}}}}$$

If 'n' is the fraction of full load KVA at which the eff. of transformer is max, then,

$$\text{Iron loss} = P_i$$

$$\text{Copper loss} = x^2 P_c$$

For max. eff.

$$x^2 P_c = P_i$$

$$\Rightarrow x = \sqrt{\frac{P_i}{P_c}} \quad \text{KVA load}$$

Output KVA corresponding to max. efficiency = $n \times \text{full load KVA}$

$$\% \eta_n = \frac{x n \text{KVA} \times 1000 \times \cos \phi}{x n \text{KVA} \times 1000 \times \cos \phi + P_i + x^2 P_c} \times 100$$

Q-1 In a 25 KVA, 2000 V power transformer has iron & full load Cu losses of 350W & 400W respectively. Calculate the efficiency at unity power factor at:-

- (i) full load
- (ii) half load

Ans:-

$$(i) \eta = \frac{1 \times 25 \times 1000 \times 1}{1 \times 25 \times 1000 \times 1 + 350 + 1 \times 400} \times 100 = \frac{2500}{2500 + 75} \times 100 = 97.98\%$$

$$\text{Given: } x = \frac{1}{2} \quad \text{and} \quad S_{\text{od}} = 500$$

$$(ii) \eta = \frac{\frac{1}{2} \times 25 \times 1000 \times 1}{\frac{1}{2} \times 25 \times 1000 \times 1 + 350 + \frac{1}{4} \times 400}$$

$$= \frac{1250}{1250 + 45} = 96.52\%$$

Q-2) In a 50 kVA, 1100 V transformer, the iron & full load Cu losses are 350W & 425W respectively.

calculate the efficiency at

full load with unity power factor

half load

full load with 0.8 PF lagging

Sol:-

$$(i) \eta = \frac{1 \times 50 \times 1000 \times 1}{50 \times 1000 + 350 + 400} = \frac{5000}{5000 + 750} = 98.59\%$$

$$(ii) \eta = \frac{\frac{1}{2} \times 50 \times 1000 \times 1}{\frac{1}{2} \times 50 \times 1000 + \frac{350}{2} + \frac{1}{4} \times 400} = \frac{25 \times 100}{25 \times 100 + 35 + 10,625} = \frac{2500}{2500 + 45} = 98.20\%$$

$$(iii) \eta = \frac{0.8 \times 1 \times 50 \times 1000 \times 0.8}{50 \times 1000 \times 0.8 + 350 + 400} = 98.1\%$$

(iv) determine the max. efficiency & load at which max. eff. occurs. (assuming load to be resistive i.e. $\cos \phi = 1$)

Sol:-

at which, $x = \sqrt{\frac{P_i}{P_c}} = \sqrt{\frac{350}{425}}$

$x = 0.907$

Camlin	Page
Date	/ /

$\chi = 90.7\% \text{ of full load KVA}$

$$\begin{aligned} \text{o/p KVA at which eff will be max}^m &= \alpha \times \text{full load KVA} \\ &= 0.907 \times 50 \times 10^3 \\ &= 45.35 \times 10^3 \end{aligned}$$

$$\% \eta_{\max.} = \frac{1 \times 45.35 \times 10^3 \times 1}{1 \times 45.35 \times 10^3 + 350 + 350} = 98.4\%$$

Q-3) The eff. of a 400 KVA single phase transformer is 98.77%, when delivering full load at 0.8 PF lagging and 99.13%. at half load & unity r.f. calculate:-

(i) Iron loss

(ii) Core loss

Sol:-

$$98.77 = \frac{1 \times 400 \times 1000 \times 0.8}{1 \times 400 \times 1000 \times 0.8 + P_i + P_c} \times 100$$

$$98.77 = \frac{32 \times 10^6}{32 \times 10^4 + P_i + P_c}$$

$$3160.64 \times 10^4 + 98.77 (P_i + P_c) = 32 \times 10^6$$

$$P_i + P_c = \frac{393600 - 3985}{98.77}$$

$$\frac{99.13}{100} = \frac{\frac{1}{2} \times 200 \times 1000 \times 1}{\frac{1}{2} \times 400 \times 1000 + P_i + \frac{P_c}{4}}$$

$$0.9913 = \frac{2 \times 10^5}{2 \times 10^6 + P_i + \frac{P_c}{4}}$$

$$1.9826 \times 10^{15} + 0.9913 \left[P_i + \frac{P_c}{4} \right] = 2 \times 10^6$$

$$\frac{P_i + P_c}{4} = \frac{17400}{0.9913} = 17552.7$$

3985 - $P_i = 1012.0 \text{ W}$
 $P_c = 2973 \text{ W}$

→ All day efficiency :-

It is defined as ratio of the output in kWh to input in kWh for 24 hrs.

$$\% \text{ All day eff} = \frac{\text{O/P (In kWh)}}{\text{I/P (In kWh)}} \text{ for 24 hrs}$$

Q-1) A 20 kVA transformer on domestic load;

which can be taken as of unity P.F., has a full load efficiency of 95.3%, the Cu loss being twice iron loss. Calculate its all day eff. on full load cycle.

No load $\Rightarrow 10 \text{ hrs}$

Half load $\Rightarrow 8 \text{ hrs}$,

full load $\Rightarrow 6 \text{ hrs}$.

Sol:-

Full load -

$$\rightarrow \text{O/P in kW} = 20 \times 1 = 20 \text{ kW}$$

Full load in I/P:-

$$(kW) = \frac{\text{O/P}}{\eta} = \frac{20}{95.3} \times 100 = 20.986 \text{ kW}$$

$$\rightarrow \text{Total losses} = P_i + P_c = 20.986 - 20$$

$$P_i + P_c = 0.986 \text{ kW} \quad \text{--- (1)}$$

$$P_c = 2P_i \quad \text{--- (2)}$$

$$P_i = 0.328 \text{ kW}$$

Full load Cu losses, $P_c = 0.6574 \text{ kW}$

$$\rightarrow \text{kWh o/p in 24 hrs} = 0 + \frac{1}{2} \times 20 \times 8 + 1 \times 20 \times 6 \\ = 200 \text{ kWh}$$

Numerically, All day off, voltage regulation $\rightarrow V_{\text{imp}}$.
testing

Camlin	Page
Date	1

$$\rightarrow \text{Iron losses for 24 hrs} = 0.3287 \times 24 = 7.89 \text{ kWh}$$

$$\rightarrow \text{Cu loss for 24 hrs} = 0 + \left(\frac{1}{2}\right)^2 \times 0.6574 \times 8 + (1)^2 \times 0.6574 \times 6 \\ = 5.259 \text{ kWh}$$


$$\rightarrow \text{Input in 24 hrs.} = \text{Output (in kWh) for 24 hrs} + \text{Losses (in kWh)} \\ \text{for 24 hrs.} \\ = 200 + 7.89 + 5.259 \\ = 213.149 \text{ kWh}$$

$$\% \text{ if all day} = \frac{\text{O/P (in kWh)} \text{ for 24 hrs.}}{\text{T/P (in kWh)}} \\ = \frac{200}{213.149} \times 100 = 93.83\%$$

Testing of Transformer:-

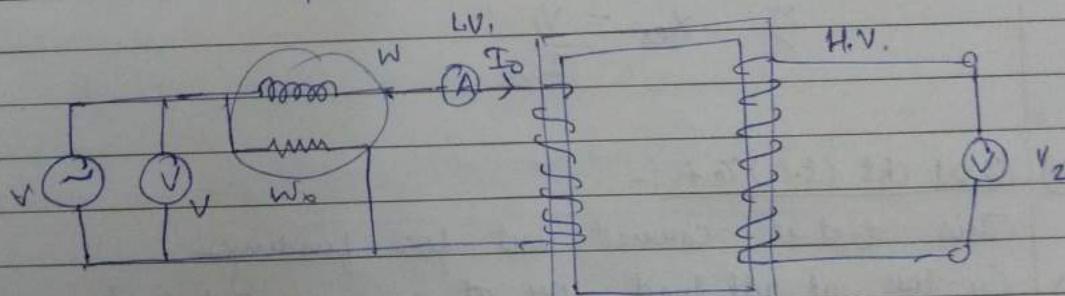1) O.C. or No load Test :-

This test is carried out to find no load iron losses and no load current I_0 which is helpful in finding no load parallel branch parameters R_0 and X_0 .



This test is usually carried out on low voltage side i.e. an wattmeter, voltmeter are connected on low voltage side. The primary winding (low voltage winding) is connected to an

voltage with normal freq & sec side should left open
connected with a voltmeter

Since, the secondary (High voltage winding) is open, the current drawn by the primary no load current I_0 measured by ammeter. As the value of no load current I_0 is very small, the Cu losses in primary & secondary winding are negligible. \therefore Wattmeter reads iron or core loss.

Let wattmeter reading = W_0 , voltmeter reading = V_1 , & ammeter reading = I_0 . Then iron loss in the transformer is $\frac{W_0}{V_1 I_0 \cos \phi_0}$.


$$P_i = W_0$$

$$V_1 I_0 \cos \phi_0 = W_0$$

$$\text{No load PF } \cos \phi_0 = \frac{W_0}{V_1 I_0}$$

$$I_w = \frac{W_0}{V_1} = I_0 \cos \phi_0$$
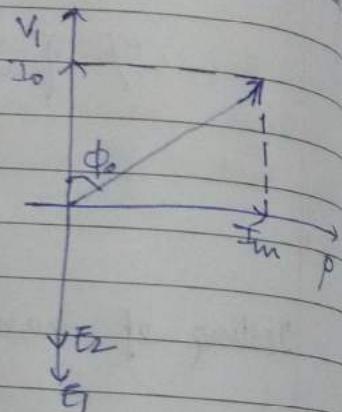
$$I_m = \sqrt{I_0^2 - I_w^2} = I_0 \sin \phi_0$$



2) No load parameters:


$$1) R_{es} = \frac{V_1}{I_w}$$

$$2) X_{es} = \frac{V_1}{I_m}$$

2) Short ckt (S.C) Test :-

This test is carried out for finding -

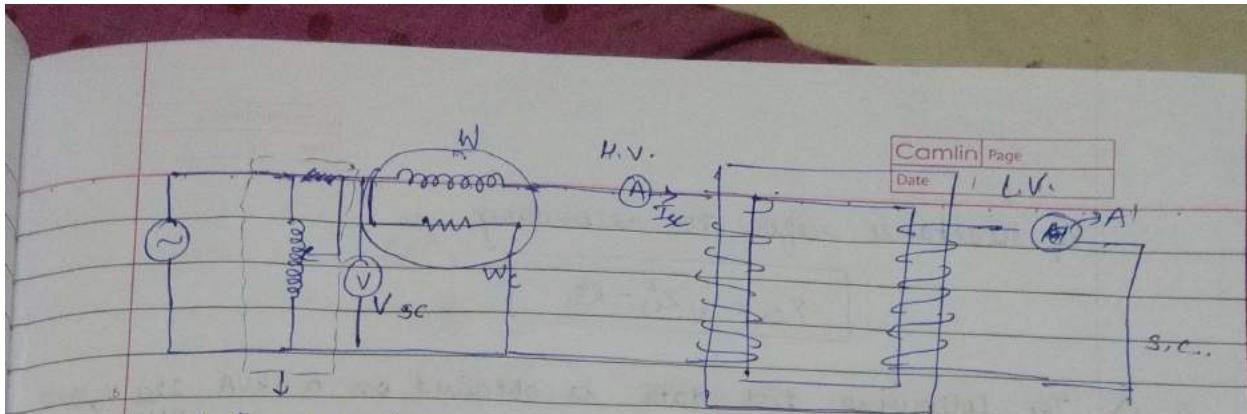- 1) Cu-loss at full load or at any desired load
- 2) Equivalent Impedance (Z_{es} or Z_{ep}), Eq. resistance (R_{es} or R_{ep}) and Equivalent leakage reactance (X_{es} or X_{ep})



Auto transformer

This test is gen. carried out on high v side A, V, W are connected on S LV winding in sickled leg a thick strip or leg connecting an ammeter. The HV winding is supplied with A.C voltage with normal frequency along with an auto transformer so that full load current gradually flows in both the windings which are measured by ammeters A and A₁. LV winding is essential for HV winding, failing which an excessive current will flow in both the windings which may damage them. As we apply low voltage, flux set up in the core will also be very small, therefore iron losses would be negligible. Therefore wattmeter reading only shows Co loss.

Let wattmeter reading be W_c ,

A reading be I_{sc} & V reading be V_{sc} .

\therefore Full load Co loss will be given by:

$$P_c = I_{sc}^2 R_{es}$$

\therefore P_c, R_{es} refer to secondary.

$$R_{es} = \frac{P_c}{I_{sc}^2} = \frac{W.R.}{A.F}$$

$$\text{Now, } V_{sc} = I_{sc} Z_{es}$$

Eq. Impedance refer to sec.

$$Z_{es} = \frac{V_{sc}}{I_{sc}} = \frac{V.R.}{A.R.}$$

Eq. reactance refer to secondary

$$X_{es} = \sqrt{Z_{es}^2 - R_{es}^2}$$

Q-1) The following test data is obtained on a 5kVA, 220V / 440V single phase transformer.

O.C. test \rightarrow 220V, 2A, 100W (LV) $\rightarrow P_i$

S.C. test \rightarrow 40V, ~~H.F.I~~ 11.4A, 200W (HV) $\rightarrow P_o$

Determine % eff & % voltage regulation at full load, at 0.9 PF lagging.

Soln:-

$$\eta = \frac{1 \times 5 \times 1000 \times 0.9}{1 \times 5 \times 1000 \times 0.9 + 100 + i^2 \times 200}$$

$$= \frac{4500}{4500 + 300} = 93.75\%$$

$$11.4 \left[\frac{220 \times 0.9 + 220 \times 0.9}{11.4} \right] R_{es} = \frac{220}{2} = 110$$

$$11.4 \left[\frac{200}{(11.4)^2} \times 0.9 + 3.14 \times 0.435 \right]$$

$$\frac{200}{(11.4)}$$

$$11.4 \times \left[1.54 \times 0.9 + 3.14 \times 0.435 \right]$$

$$Z_{es} = \frac{200}{11.4} = 18.2$$

$$R_{es} = 1.53$$

Comin	Page
Date	/ /

$$R_{ds} = \frac{W}{(A)^2} = 1.539 \Omega$$

$$Z_{ds} = \frac{V}{I} = 3.509 \Omega$$

$$X_{ds} = \sqrt{Z_d^2 - R_{ds}^2} = 3.153 \Omega$$

$$\cos \phi = 0.9$$

$$\sin \phi = 0.425$$

$$\% VR = \frac{11.4}{V_S} (R_m \cdot \cos \phi + X_m \sin \phi)$$

↓ 440

$$\% VR = 7.2\%$$

- Q- Write a short note on Auto-transformer.
 (Prepare for 10 marks).

Camlin Page
Date / /

CIRCUIT ANALYSIS TOOLS

circuit & Network-

Every circuit is a network but not vice versa.

1) Circuit:-

A conducting path through which an electric current either flows or is intended to flow is called a circuit.

2) Linear circuit-

A circuit whose parameters (R, L, C) are constant or obey Ohm's law is called a linear circuit.

3) Non-linear circuit -

A circuit whose parameters change with voltage or current or does not obey Ohm's law is called Non-linear circuit.

4) Unilateral circuit:-

A unilateral circuit whose properties or characteristics change with the direction of its operation is called Unilateral circuit.

5) Bilateral circuit :-

A circuit whose properties or characteristics remain same in either direction is called Bilateral circuit.



6) Active circuit:-

A circuit which contains one or more than one source is called an active circuit.

7) Passive circuit:-


A circuit which does not contain any source of emf is passive circuit.

8) Node:-

It is a junction in a circuit where 2 or more line elements are connected together.

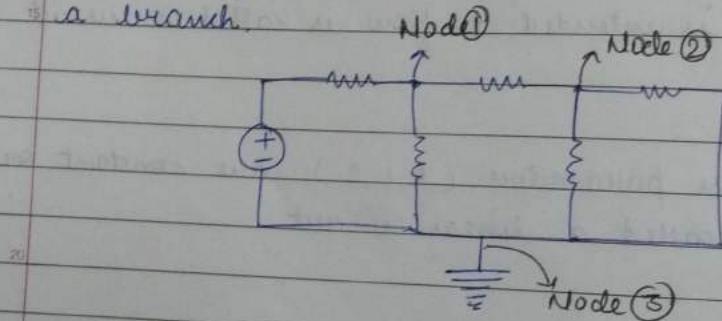9) Branch:-


The part of a ckt. which lies b/w two junction is called a branch.



KCL :-

① It states that the sum of current entering a junction equal to sum of currents leaving the junction.

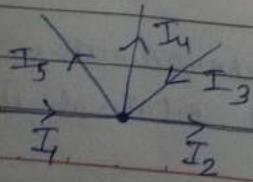② If the current towards the junction is considered positive those away as negative then the algebraic sum of all currents meeting at a common junction is zero.



$$I_1 + I_3 = I_2 + I_4 + I_5$$

$$I_1 + I_3 - I_2 - I_4 - I_5 = 0$$

No. of equations = (Nodes - 1)



Camlin Page
Date / /

KVL :-


- It states that the sum of emf around any closed loop of a circuit equals the sum of potential drop in that loop.
- If rise in voltage is considered positive and drop in voltage as negative, then the algebraic sum of potential difference around a closed loop is zero.

$E = i_1 R_1 + i_2 R_2$

$E - i_1 R_1 - i_2 R_2 = 0$

No. of equations = No. of loops

→ No. of eqn's formed in KCL are always less than eqn's formed in KVL.

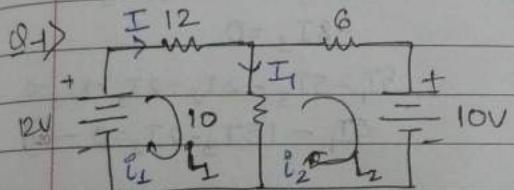
Q-1) 

$i_2 = 12i_1$ KVL

Method $12 = 12i_1 + 10i_1$,
 $i_2 = 6(i_1 - i_2) + 10i_1$

Method I $12i_1 + 10(i_1 - i_2) = 12$
 II $6i_2 + 10(i_2 - i_1) = -10$

Or directly $22i_1 - 10i_2 = 12$,
 $16i_2 - 10i_1 = -10$

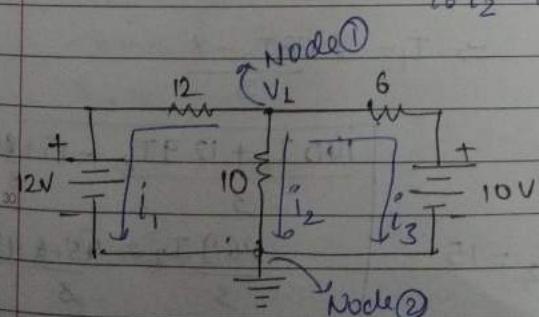Node(1) 

$i_1 + i_2 + i_3 = 0$

$\frac{V_1 - 12}{12} + \frac{V_1 - 10}{10} + \frac{V_1 - 6}{6} = 0$

$5V_1 - 60 + 6V_1 + 10V_1 - 100 = 0$

$21V_1 = 160 \Rightarrow V_1 = \frac{160}{21} = 7.62$



$i_1 = \frac{V_1 - 12}{12} = \frac{7.62 - 12}{12} = -0.365$
 $i_2 = \frac{V_1}{10} = \frac{7.62}{10} = 0.762$
 $i_3 = \frac{V_1 - 10}{6} = \frac{7.62 - 10}{6} = -0.3967$

Q-2) Find I_1, I_2, I_3 .

SOL:-

KVL:-

$3I_1 + 8I_3 - 4I_2 = 0$
 $5(I_1 - I_3) + -2(I_2 + I_3) = 0$
 $-8I_3 = 0$
 $5I_1 - 5I_3 - 2I_2 - 2I_3 = 0$
 $5I_1 - 15I_3 - 2I_2 = 0$

$2 = 4I_2 + 2I_2 + 2I_3$
 $2 = 4I_2 \quad 2 = 6I_2 + 2I_3$
 $I = 3I_2 + I_3$
 $I_3 = 1 - 3I_2$

$3I_1 + 8(1 - 3I_2) - 4I_2 = 0$
 $3I_1 + 8 - 24I_2 - 4I_2 = 0$
 $3I_1 - 28I_2 + 8 = 0$
 $5I_1 - 15(1 - 3I_2) - 2I_2 = 0$
 $5I_1 - 15 + 45I_2 - 2I_2 = 0$
 $5I_1 + 43I_2 - 15 = 0$
 $\frac{5}{3}[28I_2 - 8] + 43I_2 = 15$

$\Rightarrow I_1 = \frac{8}{3} \frac{28I_2 - 8}{3}$

$140I_2 + 129I_2 = 15$
3
$\frac{269}{3}I_2 = \frac{45}{3}$
$I_2 = \frac{885}{269} = 0.33$



ELECTRICAL ENGINEERING [TS]

CREDIT TO ASHISH JAIN

Camlin Page
Date: _____

$$I_1 = \frac{28I_2 - 8}{3} = \frac{28 \times 0.197 - 8}{3} = \frac{31.6}{3} = 0.828 = 0.283$$

$$I_3 = 1 - 3I_2 = 1 - 3 \times 0.197 = \frac{31.6}{8} = 0.409 = 0.052$$

KCL:-

$$I_1 = I_2 + I_3$$

$$\frac{V_1 - V_2}{8} + \frac{V_1 - V_3}{3} + \frac{V_3}{2} = 0$$

$$(V_1 - 2) + \frac{V_1 - V_3}{3} = I_1 + \frac{V_3}{2}$$

$$\frac{V_2 - V_1}{8} + \frac{V_2 - V_3}{4} + \frac{V_3}{2} = 0$$

$$7V_1 + 5V_2 - 80 = 0$$

$$V_2 - V_1 + 2V_2 - 4 + 4V_2 = 0 \Rightarrow 7V_2 - V_1 = 4 \quad \text{--- (2)}$$

$$V_1 = 7V_2 - 4$$

$$18(7V_2 - 4) - 5V_2 = 10$$

$$126V_2 - 72 - 5V_2 = 10 \Rightarrow 121V_2 = 82 \Rightarrow V_2 = 0.67$$

$$V_1 = 7 \times 0.67 - 4 = 0.739V$$

$$I_1 = \frac{V_1 - 2}{3} = \frac{15V_1 - 15V_2 + 40V_1 - 80 + 24V_1}{120} = 0$$

$$I_1 = \frac{V_1 - 2}{3} = \frac{79V_1 - 15V_2}{120} = 0 \quad \text{--- (1)}$$

$$I_2 = \frac{V_2 - 2}{4} = \frac{0.736 - 2}{4} = -0.316A$$

$$553V_2 - 316 - 15V_2 = 80$$

$$V_2 = \frac{396}{538} = 0.736V$$


$$I_3 = \frac{V_1 - V_2}{8} = \frac{0.736 - 0.739}{8} = 0.052A$$

$$V_1 = 7 \times 0.736 - 4 = 1.152V$$



Superposition Theorem :-

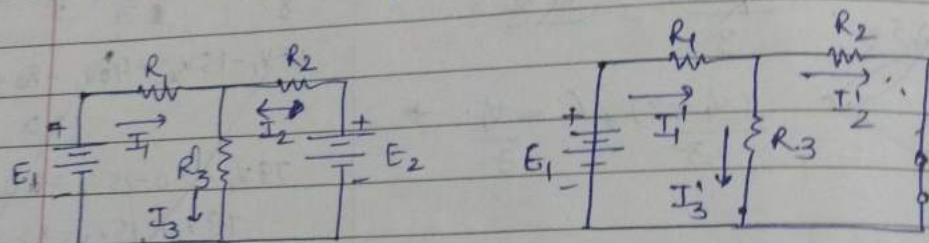It states that in any linear bilateral network containing more than one source of emf then the current in any branch is the algebraic sum of a number of individual currents considering the emf's separately and replacing other sources by their internal resistances.




$$R_{\text{eq}}' = \frac{R_1 + R_2 R_3}{R_2 + R_3}$$

$$I_1' = \frac{E_1}{R_{\text{eq}}'}$$

$$I_2' = \frac{R_3}{R_2 + R_3} \cdot I_1'$$

$$I_3' = \frac{R_2}{R_2 + R_3} I_1'$$

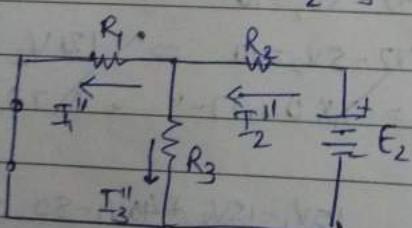

$$R_{\text{eq}}'' = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$

$$I_1'' = \frac{E_1}{R_{\text{eq}}''}$$

$$I_2'' = \frac{R_3}{R_1 + R_3} I_1''$$

$$I_3'' = \frac{R_1}{R_1 + R_3} I_1''$$

$$I_L = |I_1'| - |I_1''|$$



Thevenin's Theorem :

It is used to determine the current through load resistor R_L connected across two terminals of a network which contains voltage sources and resistors, then the network can be replaced by a single source of emf called V_{Th} & a series resistor R_{Th} where V_{Th} is P.D. when R_L is removed & R_{Th} is eq. resistance as seen from the terminals under consideration.

R_L, V_{Th}, R_{Th}

$i = \frac{V}{R_1 + R_3}$


$V_{TA} = \frac{R_3}{R_1 + R_3} V$

$R_{Th} = \frac{R_2 + R_1 R_3}{R_1 + R_3}$


$$i_L = \frac{V_{Th}}{R_{Th} + R_L}$$


Norton's Theorem :-

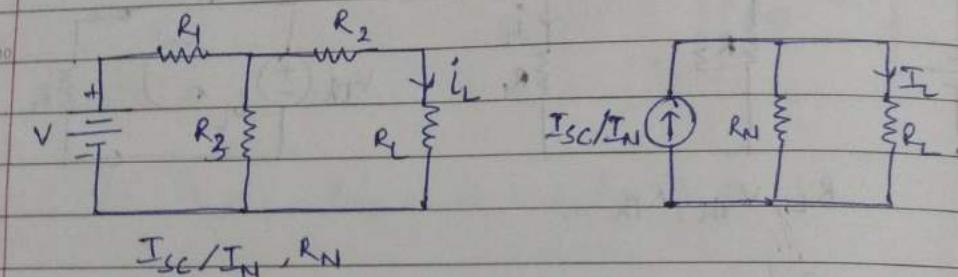It is used to find current flowing through the load in any linear bilateral network containing independent voltage and current source may be replaced by an equivalent current source I_N in parallel with the resistance R_N where I_N is the short circuit current I_{SC} and R_N is equivalent resistance as seen from the terminals under consideration.



$$I_{SC}/I_N, R_N$$

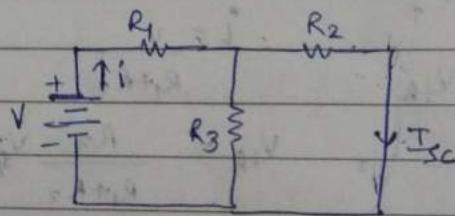

$$Req. = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$i = \frac{V}{Req.}$$

$$I_{SC} = \frac{R_3}{R_2 + R_3} i$$

$$R_N = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$

$$I_L = \frac{R_N}{R_N + R_L} \cdot I_{SC}$$

Camlin Page
Date / /

Use Thevenin's Theorem.

$V_{Th} = \frac{24 \times 48}{6+24+2} = \frac{24 \times 48}{32} = \frac{24 \times 48}{32} = 36V$

$R_{Th} = \frac{8 \times 24}{32} = 6\Omega$

$i = \frac{48}{32}$, $i_L = \frac{36}{30+6} = 1A$

Apply Norton's Theorem

$R_N = 10 + \frac{8 \times 12}{8+12} = 10 + \frac{96}{20} = 10 + 4.8 = 14.8\Omega$

$i = \frac{20 \times 11}{14.8} = \frac{220}{14.8} = 14.8A$

Camlin Page
Date / /

$$I_{sc} = \frac{20}{8} = 2.5A$$

$$R_N = \frac{8 \times 24}{8+24} = \frac{192}{32} = 6\Omega$$

$$i_L = \frac{R_N I_{sc}}{R_N + R_L} = \frac{6}{6+12} \times 2.5 = \frac{6}{18} \times 2.5 = \frac{25}{30} = \frac{5}{6} A = 0.83A$$

(Q-3)

Apply Thevenin's Theorem.

Sol:-

$$I = \frac{12}{18} = \frac{2}{3} A$$


$$V_A = \frac{2}{3} \times 12 = 8V$$

$$V_B = 5 \times 4 = 20V$$

$$V_{TA} = 8 - 20 = -12V$$

For finding V_{th} , R_L short.

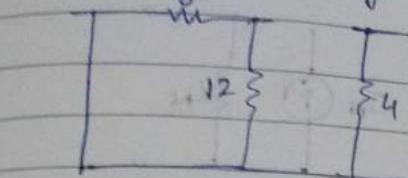for finding R_{TH} , voltage source short.




$$\frac{6+12 \times 4}{12+4}$$

$$6 + \cancel{\frac{12 \times 4}{12+4}} \cancel{+ 4}$$


$$6 + 4 = 10 \Omega$$

$$I_c = 0.75A$$
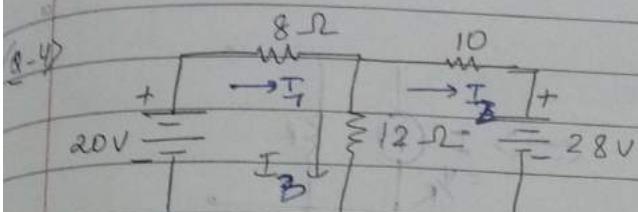
$$R_{TH} = 6.21 \frac{6 \times 12}{8+12} + 4 = \frac{6 \times 12}{18} + 4 = 8 \Omega$$



Apply Superposition
Theorem.

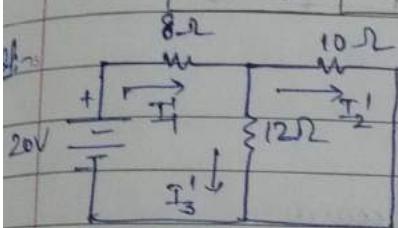


$$R_{eq}' = 8 + \frac{12 \times 10}{22} = \frac{88+60}{11} = \frac{148}{11} \Omega$$

$$I_1' = \frac{10}{20 \times 11} = \frac{110}{220} = \frac{55}{37} A = 1.486 A$$

$$I_2' = \frac{12}{22} \times \frac{55}{37} = \frac{30}{37} A = 0.811 A$$
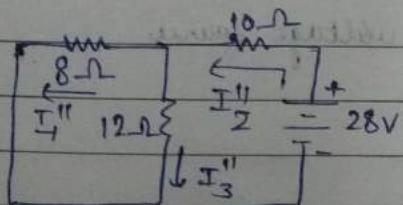
$$I_3' = \frac{5}{22} \times \frac{55}{37} = 2.5 A = 0.676 A$$



$$R_{eq}'' = 10 + \frac{8 \times 12}{20} = \frac{50+24}{5} = \frac{74}{5} \Omega$$

$$I_2'' = \frac{20}{28} \times \frac{85}{37} = \frac{85}{37} A = 2.297 A$$

$$I_1'' = \frac{3}{20} \times \frac{88}{37} = \frac{57}{37} A = 1.378 A$$


$$I_1 = 1.486 - 1.378 = 0.108 A$$

$$I_2 = 0.676 + 0.919 = 1.595 A$$

$$I_3'' = \frac{28}{20} \times \frac{85}{37} = \frac{34}{37} A = 0.919 A$$

$$I_3 = I_2 - I_1 = 0.811 - 1.378 = -0.567 A$$


Dual Network (Thévenin & Norton) :-

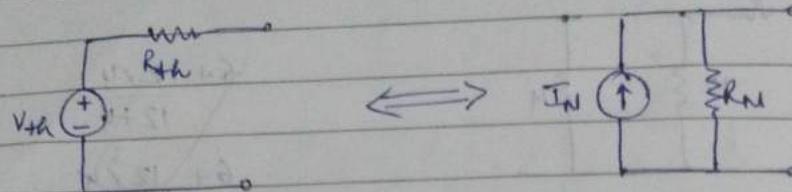

(Source Conversion)

Voltage source \rightarrow Current source and vice-versa
 Resistance in series \leftrightarrow Resistance in parallel

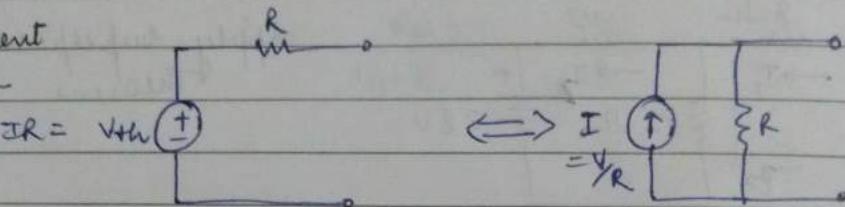
Independent sources -
 Voltage $IR = V_{th}$ & Current




(Two source types)

Dependent sources:-

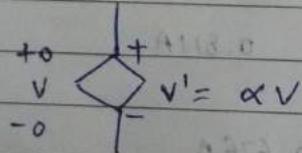
1) VDVS - Voltage dependent voltage source



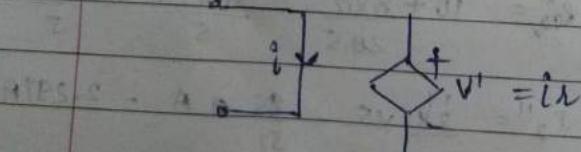
2) CDVS - Current dependent voltage source



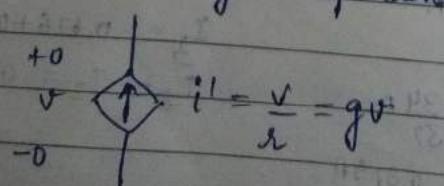3) VDCS - Voltage dependent current source




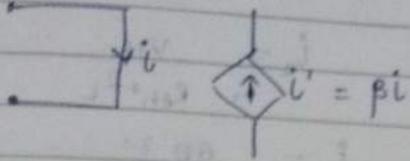Q) CDGS - Current dependent current source.



Maximum Power Transfer Theorem:-

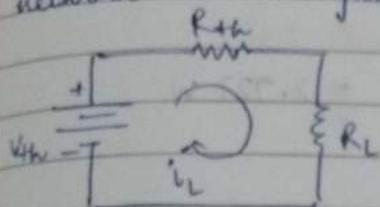Max^m power output is obtained from a network when the load resistance is equal to the internal resistance of the network as seen from the terminals of the load.




$$R_L = R_{th} \rightarrow \text{Max. Power}$$

$$Z_{th} = 10 + 10j$$

$$Z_{th} = R + jX$$

$$Z_L = R - jX$$

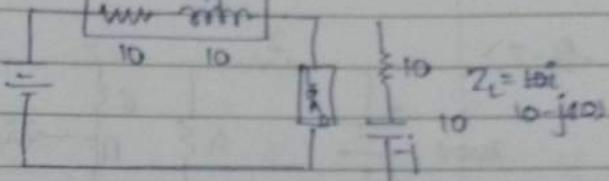


$$P_L = I_L^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

$$\frac{dP_{max.}}{dR_L} = 0$$


The condⁿ $R_L = R_{th}$ is derived from this eqⁿ.

$$P_{max.} = \frac{V_{th}^2}{4R_L}$$

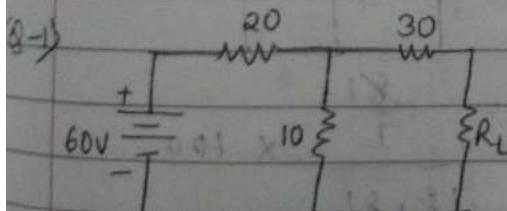


(i) Find the current through R_L where it takes values of 5Ω & 25Ω .

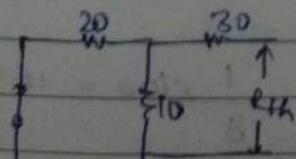(ii) Also calculate R_L for which the power dissipated in it would be max^m & also find this power.



$$R_{th} = 30 + \frac{20 \times 10}{30} = \frac{90 + 20}{3} = 110 \Omega$$

$$= 33.333 \Omega$$

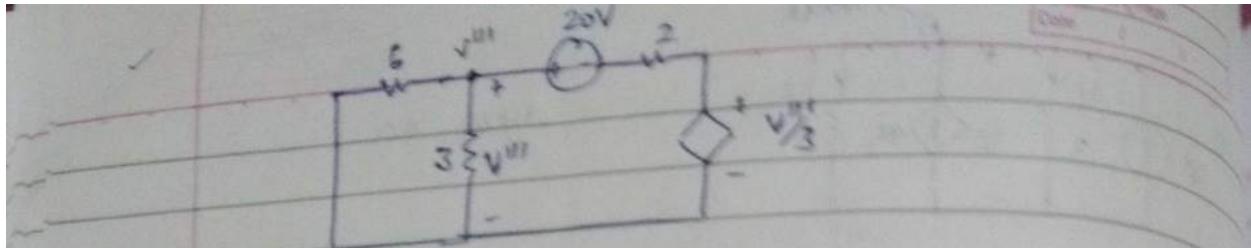


$$\frac{V^{111}}{6} + \frac{V^{111}}{3} + \frac{V^{111} - 20 - \frac{V^{111}}{3}}{2} = 0$$

$$\frac{V^{111}}{6} + \frac{V^{111}}{3} + \frac{2V^{111} - 60}{6} = 0$$

$$V^{111} + 2V^{111} + 2V^{111} - 60 = 0$$

$$V^{111} = +12V$$

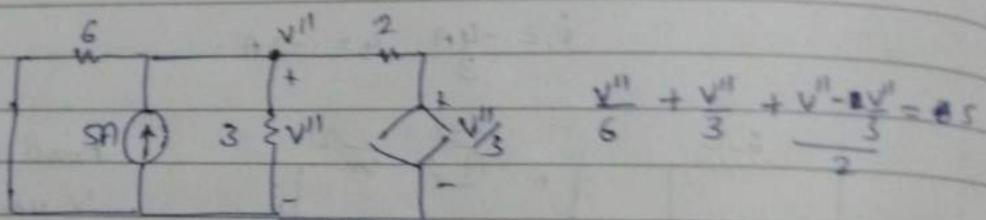

$$\frac{V^{111}}{6} + \frac{V^{111}}{3} + \frac{V^{111} - 2V^{111}}{3} = 5$$

$$V^{111} + 2V^{111} + 2V^{111} = 30$$

$$V^{111} = 6V$$

$$V = 6 + 6 + 12 = 24V$$

Dependent Source Thevenin's Theorem:-

- For both dependent & independent source -
i) find V_{th} across terminal AB (load)
ii) for R_{th} short circuit AB terminal & find $I_{sh} \rightarrow$ (short current) & then find R_{th} , as $R_{th} = \frac{V_{th}}{I_{sh}}$
- For dependent sources only -
i) In this case V_{oc} (open ckt voltage) = 0

ELECTRICAL ENGINEERING [TS]

CREDIT TO ASHISH JAIN

(Page No. _____ Date _____)

$$I_{sh} = \frac{12}{\frac{4+2}{6}} = \frac{12}{6} = 2 \text{ A}$$

$$I_{sh} = \frac{4}{3} \text{ A}$$

$$R_{th} = \frac{V_{th}}{I_{sh}} = \frac{8 \times 3}{4} = 6 \Omega$$

(B-3) Find out Thevenin's equivalent circuit.

$$6 - V_{th} = 9i + \frac{V_{th}}{10}$$

$$i = \frac{6 - V_{th}}{100}$$

put this value of i in eqn ①

$$-i + \frac{V_{th}}{10} = 9i$$

$$V_{th} = 10 \times 8i = 80i$$

$$100i = 80i - 6$$

$$20i = -6 \Rightarrow i = -\frac{3}{10} \text{ A}$$

$$100i = 6 - 100i$$

$$200i = 6$$

$$i = \frac{6}{200} \text{ A}$$

$$V_{th} = -80 \times \frac{3}{10} = -24 \text{ V}$$

$$V_{th} = 3 \text{ V}$$

$$I_{sh} = i + 9i = 10i = -\frac{3}{10} \text{ A}$$

$$R_{th} = \frac{-24}{3} = 8 \Omega$$

$$R_{th} = \frac{3}{3} \times 10 = 10 \Omega$$

Final answer should be in Polar form.

Camlin	Page
Date	/ /

A.C. Circuits :-

Rectangular Form:-

$$x+iy$$

$$(+, -)$$

Polar Form:-

$$M \angle \theta$$

$$(X, \div)$$

$$M = \sqrt{X^2 + Y^2}$$

$$\theta = \tan^{-1} \left(\frac{Y}{X} \right)$$

$$30i_1 - 10i_2 = 100\angle 0^\circ$$

$$3i_1 - i_2 = 10\angle 0^\circ \quad \text{--- (1)} = 10$$

$$-10i_1 + 15i_2 = -50\angle 90^\circ$$

$$-2i_1 + 3i_2 = -10\angle 90^\circ \quad \text{--- (2)} = -10j$$

$$\text{eqn (1)} \times 3 + \text{eqn (2)}$$

$$7i_1 = 30 - 10j \quad 3(-2i_1) + 3(3i_1 - 10\angle 0^\circ) = -10\angle 90^\circ$$

$$7i_1 = 10\sqrt{10} \angle -18.43^\circ \quad 7i_1 =$$

$$i_1 = \frac{10\sqrt{10}}{7} \angle -18.43^\circ \quad i_2 = 3i_1 - 10 = \frac{3 \times 10\sqrt{10}}{7} \angle -18.43^\circ - 10$$

Q2)

Find the value of 'V' using Superposition principle.

Sol:-

$$Z_{eq_v} = \frac{(3+j4)(-j4)}{3+j4-j4} = \frac{-3-j12+16}{3}$$

$$Z_{eq_v} = \frac{16-4j}{3}$$

Ques. 1) Connect 1A source at terminal AB and find V_{AB} .

$R_{TH} = \frac{V_{AB}}{1A}$

Find out its Thvenin's equivalent circuit.

Ans:

$$\frac{V_{AB} - 2i}{6} + \frac{V_{AB}}{12} = 1 \quad \text{---(1)}$$

$$\frac{V_{AB}}{12} = 1 \quad \text{---(2)}$$

$$V_{AB} = 12i$$

$$\frac{12i - 2i}{6} + \frac{12i}{12} = 1$$

$$\frac{10i}{6} + 1 = 1$$

$$16i = 6$$

$$i = \frac{3}{8}$$

$$V_{AB} = \frac{3}{8} \times 12 = \frac{36}{8} = 4.5$$

Ques. 2) Find Thvenin's equivalent circuit.

Ans:

KVL: $4i + 4i = 12 + 2i$

$$6i = 12$$

$$i = 2A$$

$$V_{TH} = 2 \times 4 = 8V$$

ELECTRICAL ENGINEERING [TS]

CREDIT TO ASHISH JAIN

